



# Applied electronics

## Exam of 22 January 2021

*This is an example of exam. Solutions are reported in red in the orange rectangle.*

*Exam consists in 10 Quiz (max 10 points), 4 open problems (5 point each), 3 optional questions on lab part (1 point each)*

*Score is: (quiz points + problem points)\*0.9+optional questions points . Max mark is 30/30*

### Domanda 1

Risposta corretta

Punteggio ottenuto 1,0 su 1,0

Consider a square wave generator realized with Schmitt trigger inverter; the voltage on the capacitor varies with time as:

- ☐ (a) square wave
- ☐ (b) is always zero
- ☐ (c) linear
- ☒ (d) exponential ✓

Risposta corretta.

La risposta corretta è: exponential

**Domanda 2**

Risposta corretta

Punteggio ottenuto 1,0 su 1,0

Consider a synchronous write cycle; the STB signal must stay high for a minimum duration equal to:

- 
- ☐ (a)  $T_k + T_{txmin}$
  - ☐ (b)  $T_{su} + T_k$
  - ☐ (c)  $T_k$
  - ☒ (d)  $T_h + T_k$  ✓

Risposta corretta.

La risposta corretta è:  $T_h + T_k$

**Domanda 3**

Risposta corretta

Punteggio ottenuto 1,0 su 1,0

The maximum number of CMOS logic gates that can be connected to one CMOS logic gate of the same family is limited by:

- 
- ☐ (a) the maximum output current from the logic gate
  - ☐ (b) the voltage supply  $V_{dd}$
  - ☒ (c) the maximum acceptable delay for a logic state transition
  - ☐ (d) the maximum static power consumption



Risposta corretta.

La risposta corretta è:  
the maximum acceptable delay for a logic state transition

**Domanda 4**

Risposta corretta

Punteggio ottenuto 1,0 su 1,0

Consider a FPGA; a Look-Up Table (LUT) with 3 inputs needs:

---

- ☐ (a) 8 FAMOS
- ☐ (b) 8 NAND gates and 4 NOR gates
- ☒ (c) 8 SRAM memory cells ✓
- ☐ (d) 4 NAND gates and 8 NOR gates

Risposta corretta.

La risposta corretta è: 8 SRAM memory cells

**Domanda 5**

Risposta corretta

Punteggio ottenuto 1,0 su 1,0

A FAMOS when programmed

---

- ☒ (a) has a threshold voltage higher than the threshold voltage of the FAMOS which is not programmed ✓
- ☐ (b)  
has  $I_{DS}$  higher than the not programmed FAMOS, when same  $V_{DS}$  is applied
- ☐ (c) has a threshold voltage smaller than the threshold voltage of the FAMOS which is not programmed
- ☐ (d)  
has a threshold voltage equal to the threshold voltage of the FAMOS which is not programmed

Risposta corretta.

La risposta corretta è: has a threshold voltage higher than the threshold voltage of the FAMOS which is not programmed

### Domanda 6

Risposta corretta

Punteggio ottenuto 1,0 su 1,0

AA NAND Flash memory consists in:

- ☐ (a) NMOS and PMOS transistors in series
- ☐ (b) NMOS and PMOS transistors in parallel
- ☐ (c) FAMOS transistors in parallel
- ☒ (d) FAMOS transistors in series ✓

Risposta corretta.

La risposta corretta è: FAMOS transistors in series

### Domanda 7

Risposta corretta

Punteggio ottenuto 1,0 su 1,0

The reflection coefficient of a transmission line terminated with a termination resistance  $R_T$  equal to two times the characteristic impedance of the line, is:

- ☐ (a) 1
- ☐ (b) 1/4
- ☐ (c) 1/2
- ☒ (d) 1/3 ✓

Risposta corretta.

La risposta corretta è: 1/3

**Domanda 8**

Risposta corretta

Punteggio ottenuto 1,0 su 1,0

The output voltage of buck regulators is:

---

- ☒ (a)  $V_{out} < V_{in}$  ✓
- ☐ (b)  $V_{out} = 2 V_{in}$
- ☐ (c)  $V_{out} = V_{in}$
- ☐ (d)  $V_{out} > V_{in}$

Risposta corretta.

La risposta corretta è:  $V_{out} < V_{in}$

**Domanda 9**

Risposta corretta

Punteggio ottenuto 1,0 su 1,0

The conversion time  $T_c$  of a Successive Approximation Converter can be reduced of a factor 2 by:

- 
- ☐ (a) doubling the number of bit of the SAR
  - ☐ (b)  
none of the answers reported here is the correct one
  - ☐ (c) doubling the CK period of the SAR
  - ☒ (d) doubling the CK frequency of the SAR ✓

Risposta corretta.

La risposta corretta è: doubling the CK frequency of the SAR



### Domanda 10

Risposta corretta

Punteggio ottenuto 1,0 su 1,0

The ADC of a data acquisition system provides a  $SNR_q=65.76\text{dB}$ , whereas the total SNR is degraded of other 10dB due to the non-idealities of the other blocks. Calculate the ENOB.

- 
- ☐ (a)  $ENOB < 8$
  - ☐ (b)  $ENOB > 10$
  - ☐ (c)  $ENOB = 10$
  - ☒ (d)  $ENOB = 9$  ✓

Risposta corretta.

La risposta corretta è:  $ENOB = 9$

### Domanda 11

Completo

Punteggio ottenuto 5,0 su 5,0

**Consider 8 input channels with analog signals with bandwidth up to 30kHz. The input voltage of each channel is in the range between -0.5V and +0.5V. The signals are converted with an A/D conversion system using only one S/H and Successive Approximation ADC with dynamics 0-10V. The S/H acquisition time is 500ns and the MUX introduces a delay of 30ns.**

**Request 1:** List the building blocks of the entire acquisition system, describe the role of each block and specify the bandwidth of the anti-aliasing filters.

**Request 2:** Calculate the minimum number of bits of the ADC to have 1LSB of less than 10mV

**Request 3:** Each input signal must be sampled at a frequency of 100kHz. Calculate the CK frequency of the SAR.

---

write here your answers . Solutions are in the orange rectangle

a) List the building blocks of the entire acquisition system, describe the role of each block and specify the bandwidth of the anti-aliasing filters.

b) Calculate the minimum number of bits of the ADC to have 1LSB of less than 10mV

10 bit implies  $10/(2^{10}) \cdot 1000 = 9.76 \text{ mV} \Rightarrow N=10$

- c) Each input signal must be sampled at a frequency of 100kHz. Calculate the CK frequency of the SAR.

Sampling frequency at SH is 800kHz.  $T_s = 1/(800\text{kHz}) = 1250\text{ns}$ .

$T_s = T_{acq} + T_{mux} + T_c$   $T_c = 1250 - 500 - 30 = 720\text{ns} = NT_{ck}$   $T_{ck} = 720/10 = 7.2\text{ns} \Rightarrow f_{ck} = 1/7.2\text{ns} = 13.89\text{MHz}$

### Domanda 12

Completo

Punteggio ottenuto 0,0 su 5,0

A track of 30cm on a PCB backplane has characteristic impedance  $Z_0 = 90\Omega$  (with no load), and wave propagation speed  $u = 0,6 c$ . We need to connect to the track  $N=10$  equally spaced receivers. Each device has an input capacitance of 1pF. The line is driven on one side and closed with a matched termination on the other side.

The driver and receivers have the following electrical parameters:

$V_{oh} = 4.1 V$ ,  $V_{ol} = 0,4 V$ ,  $V_{ih} = 2,5 V$ ,  $V_{il} = 1,0 V$ ;  $V_{dd} = 4.5V$ .

#### Request 1)

Calculate the capacitance per unit length of the line without any connected device.

#### Request 2)

Calculate the characteristic impedance of the line with the connected receivers

#### Request 3)

Calculate the output resistance of the driver to drive the line in IWS mode and  $NM=0.5V$ . Include in the calculation the effect of the capacitive load.

Write here your answers, solutions are in the orange rectangle

**Request 1:**

the capacitance per unit of length is  $C=1/(Z_{\infty} \cdot u) \implies C=0.62\text{pF/cm}$

**Request 2:**

$$Z_{\infty}' = Z_{\infty} / \sqrt{1 + NCi/L \cdot C} = 72.6 \text{ ohm}$$

**Request 3:**


$$Vb(0) = Z_{\infty}' / (Z_{\infty}' + Ro) \cdot Vdd \geq Vih + NM = 3V \implies Ro \leq 36.3 \text{ ohm}$$

**Domanda 13**

Completo

Punteggio ottenuto 5,0 su 5,0

 Consider the sequential circuit shown in the figure and assume that the outputs Q1, Q2 and Q3 are initially all reset to 0 logic state. Consider the capacitor C=0.



The delays for all the components are reported below:

$T_{su} = 3 \text{ ns}$ ,  $T_h = 2 \text{ ns}$  (D-FF and JK FF) ;

$T_{ck \rightarrow Q} = 5 \text{ ns}$  (D-FF and JK FF)

NAND gate and inverters I1 and S1:  $T_{LH} = 3\text{ns}$ ,  $T_{HL} = 4 \text{ ns}$ ,

Answer the following questions:

**Request 1:**

- How many CK active edges are needed to switch Q1 to logic state 1?
- Which is the initial state of the output A
- How many CK active edges are necessary to switch the output of S1 to state 1 ?

### Request 2:

Assuming  $C=0$ , calculate the maximum CK frequency.

### Request 3:

Calculate the propagation delay for a transition LèH of the state at node A. Assume:  $C=5\text{pF}$ , the input capacitance of S1 equal to  $C_i=4\text{pF}$ ,  $R_{pu}=1\text{kohm}$  and the output resistance of I1 equal to  $R_o=100\text{ohm}$  (when output of I1 is in low state);

### Request 1:

- How many CK active edges are needed to switch Q1 to logic state 1? 2
- Which is the initial state of the output A? high state
- How many CK active edges are necessary to switch the output of S1 to state 1 ? first CK edge

Request 2:

Assuming  $C=0$ , calculate the maximum CK frequency.

$T_{ckmin} = t_{ck\_Q} + t_{dnand} + t_{su} = 12 \text{ ns}$   $f_{ckmax} = 83.3 \text{ MHz}$

Request 3:

$t_{dLH} = 0.69 \cdot (C_i + C) \cdot 1 \text{ kohm} = 6.21 \text{ ns}$

#### Domanda 14

Completo

Punteggio ottenuto 5,0 su 5,0

**A DRAM memory has the following characteristics:**

- 16 bit address: 12 bits are for row address and 4 bits are for column address.
- words are of 8 bits
- pass transistors with  $C_d = 0.5 \text{ fF}$

1. #word lines = # of rows =  $2^{12} = 4096$

2. # memory cells =  $2^{12} \cdot 2^4 \cdot 8 = 524288$

3.  $C_{bL} = 2^{12} \cdot 0.5 \text{ fF} = 2.05 \text{ pF}$

**Domanda 15- Optional on laboratory part**

Analog-to-digital and Digital-to-Analog converters:

When is it possible to observe the phenomenon of "glitches" affecting the performance of a DAC converter similar to the one realised and simulated with the LTspice software during the virtual LAB? Explain the origin of the glitch.

---

**Domanda 16 Optional on laboratory part**

Which behaviour do you expect to observe if you visualise with the Waveform Viewer of the LTspice software the voltages at the near and far end of a coaxial cable described by a transmission line model (with characteristic impedance  $Z_{inf}=50\Omega$ ) with open termination and connected to a square wave generator characterised by an internal resistance of  $R_G=50\Omega$  on the driving side?

---



**Domanda 17- Optional on laboratory part**

How can you realise and simulate with the LTSpice software a square wave signal generator based on a SN74HC14 Schmitt trigger in order to provide the clock signal for a synchronous counter such as the 4-bit CD4029 counter adopted during the virtual LAB?

---