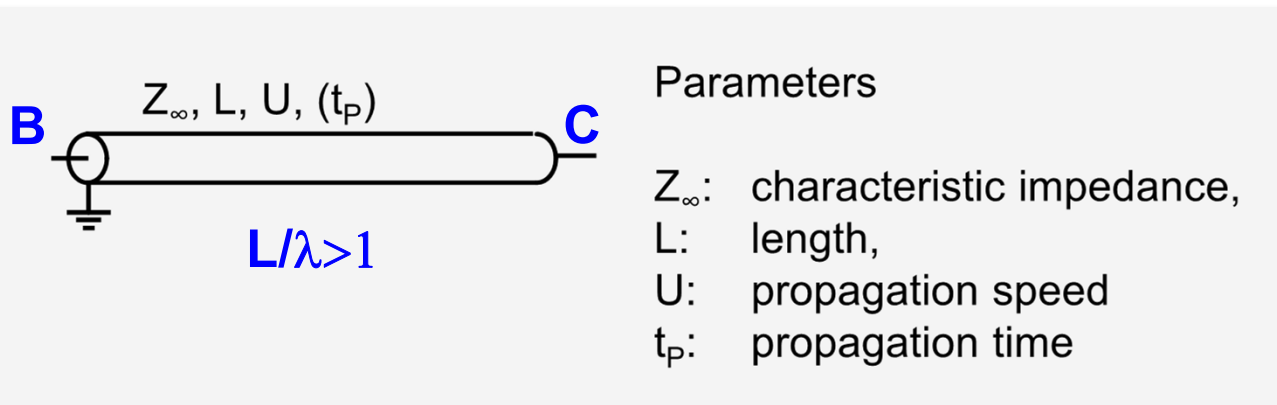



APPLIED ELECTRONICS

Part C:

Class exercises 2 with solutions on:

☐ **Transmission lines**



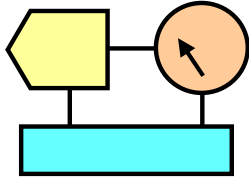


Problem 1 - Assignment


Lattice diagram

- a) Use lattice diagram to plot the voltage at the receiver $V_C(t)$ and at the driver $V_B(t)$ in a $(0 - 4 t_p)$ time range for $L \rightarrow H$ transition with V_A from 0 V to 5 V and:

$$R_G = 50 \, \Omega, \, R_T = \infty, \, Z_\infty = 50 \, \Omega, \, U = 0.8 \, c, \, L = 20 \, \text{cm}$$

- b) Repeat the calculation with $R_G = 270 \, \Omega$ and $R_G = 15 \, \Omega$

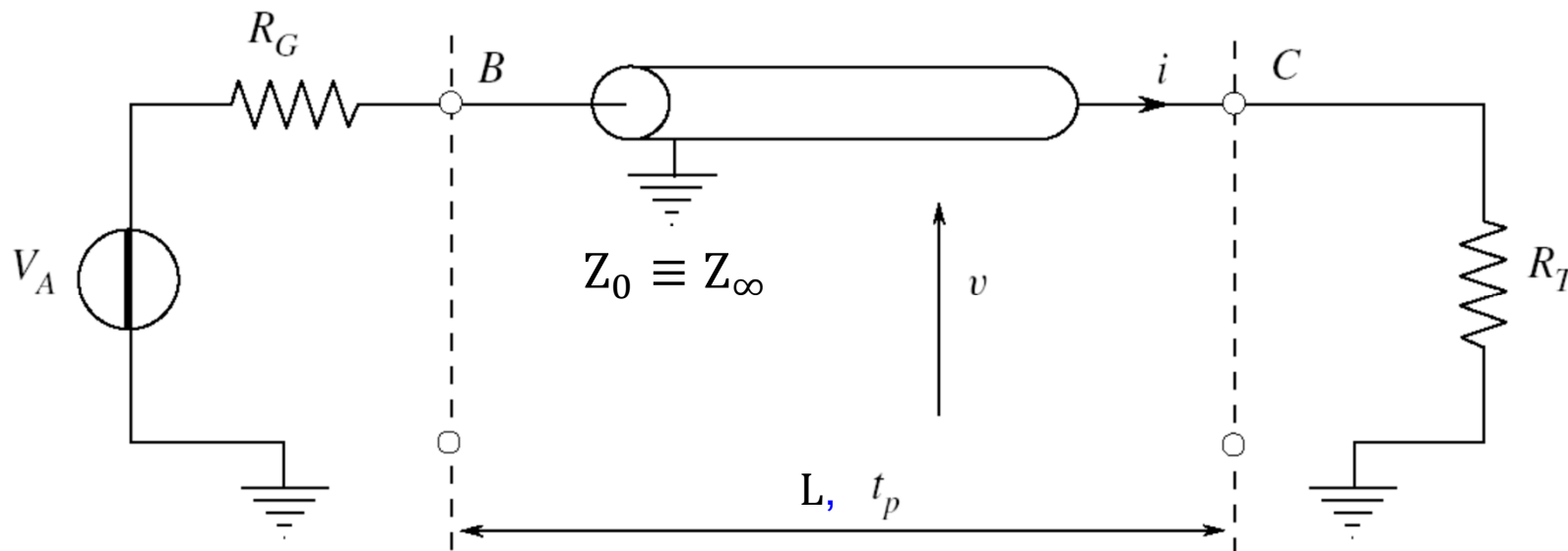

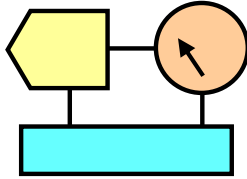

Problem 2 – Assignment

Incident Wave Switching


- a) Calculate the driver output resistance (R_O) for IWS driving for a connection with:

L \rightarrow H transition with $V_A = 0\text{ V} \rightarrow 4\text{ V}$

Receiver threshold $V_T = 2.5\text{ V}$

$Z_\infty = 70\ \Omega$ and open circuit termination

- b) Explain why this configuration can give multiple transition for a receiver placed at the far-end. Indicate how multiple transitions can be eliminated
- c) Draw qualitatively the voltage $V_C(t)$ in the case a capacitor C_L is connected at the far end.

 


Problem 3 – Assignment

Transmission times and total skew time

Consider a backplane with $L_U = 8 \text{ nH/cm}$, $Z_\infty = 85 \Omega$ (without capacitive load), length $L = 48 \text{ cm}$, open circuit termination, and 24 connectors. Each board that can be inserted in the connectors has an input capacitance of 35 pF . The system can have from 2 to 24 connected boards.

Driver/receiver CMOS: $V_{DD} = 3.3 \text{ V}$; $R_O = 95 \Omega$; $V_{IH} = 2 \text{ V}$, $V_{IL} = 1 \text{ V}$.

- Calculate t_p in the cases of 2 and 24 connected boards.
- Calculate t_{TXmin} and t_{TXmax} for 2 connected boards in the two extremes of the line
- Calculate t_{TXmin} and t_{TXmax} with 24 connected boards
- Calculate the maximum R_{OH} to drive the line in IWS mode in the case of 24 inserted boards

 


Problem 4 - Assignment

A track on a PCB backplane has characteristic impedance $Z_0 = 95 \, \Omega$ (with no load), wave propagation speed $U = 0.65 \, c$. The track length is $L = 30 \, \text{cm}$, without terminations, and 15 equally spaced devices are connected to the track. The total capacitive load of these devices increases the distributed track capacitance (towards GND) by a factor 20 (loaded unity capacitance = unloaded capacitance $\times 20$).


The interface uses CMOS circuits, with power supply $5 \, \text{V}$, and the following parameters: $V_{OH} = 4 \, \text{V}$, $I_{OH} = -16 \, \text{mA}$, $V_{OL} = 0.8 \, \text{V}$, $I_{OL} = 16 \, \text{mA}$, $V_{IH} = 2.7 \, \text{V}$, $V_{IL} = 1.3 \, \text{V}$.

Further assumptions: the PCB tracks can be considered lossless transmission lines, and linear equivalent circuits can be used for drivers and receivers.

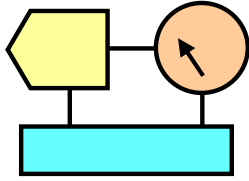

Problem 4 - Assignment

- Find the characteristic impedance Z'_0 and the propagation speed U' of the loaded track, and evaluate the propagation time t_p over the full length of the connection, for a fully loaded track.
(propagation speed $U = 1/\sqrt{L_U C_U}$)
- Find the equivalent output resistance of drivers, for H and L states (respectively R_{OH} and R_{OL}), and find the minimum and maximum transmission times t_{TXmin} and t_{TXmax} from a driver placed at one end and a receiver placed at any position along the connection, for fully loaded track without termination in case of L→H transition.
- Evaluate the equivalent driver output resistance R'_{OH} required to operate a receiver connected at any intermediate point of the track in IWS (Incident Wave Switching) for the L → H transition, with $NM = 100$ mV, and line driven from one end.
Using drivers with equivalent output resistance R'_{OH} , what should be connected at the opposite end to guarantee correct operation?

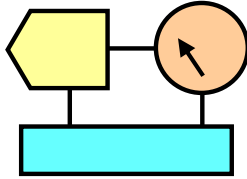

Problem 4 - Assignment

- d) Draw the Information and Control signals (INF, STB) at Driver and at Receiver, and the destination register clock CK for a **synchronous** write cycle and evaluate cycle duration with the following parameters.
- Interconnection: $t_K = 25 \text{ ns}$, $t_{TXmin} = 20 \text{ ns}$
 - Receiver register: $t_{SU} = 10 \text{ ns}$, $t_H = 5 \text{ ns}$
- e) Draw the Information and Control signals (INF, STB, ACK) at Driver and at Receiver, and the destination register clock CK for an **asynchronous** transfer cycle and evaluate cycle duration with the following parameters.
- Interconnection: $t_K = 25 \text{ ns}$, $t_{TXmin} = 20 \text{ ns}$
 - Receiver register: $t_{SU} = 10 \text{ ns}$, $t_H = 5 \text{ ns}$