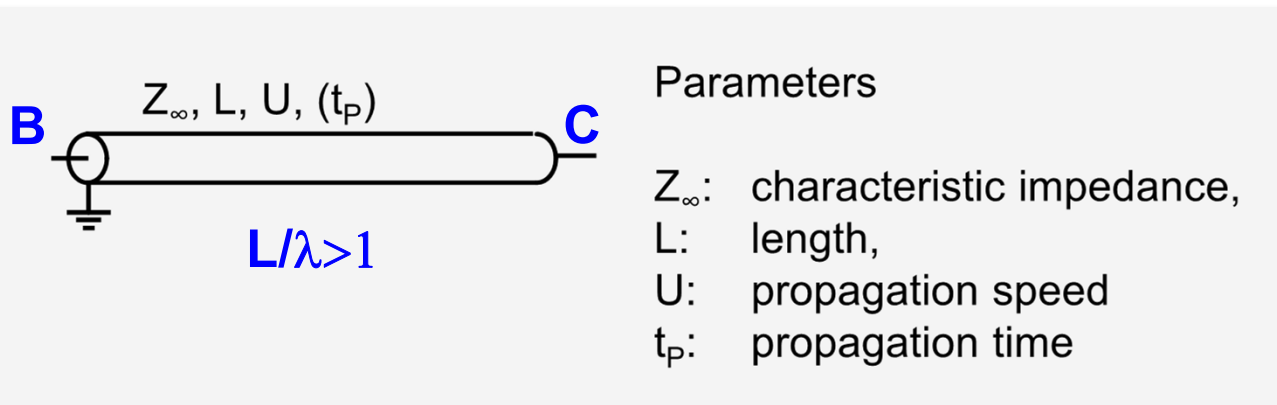



APPLIED ELECTRONICS

Part C:

Class exercises 2 with solutions on:

☐ **Transmission lines**



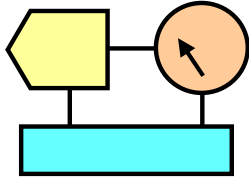


Problem 1 - Assignment


Lattice diagram

- a) Use lattice diagram to plot the voltage at the receiver $V_C(t)$ and at the driver $V_B(t)$ in a $(0 - 4 t_p)$ time range for $L \rightarrow H$ transition with V_A from 0 V to 5 V and:


$$R_G = 50 \, \Omega, \, R_T = \infty, \, Z_\infty = 50 \, \Omega, \, U = 0.8 \, c, \, L = 20 \, \text{cm}$$

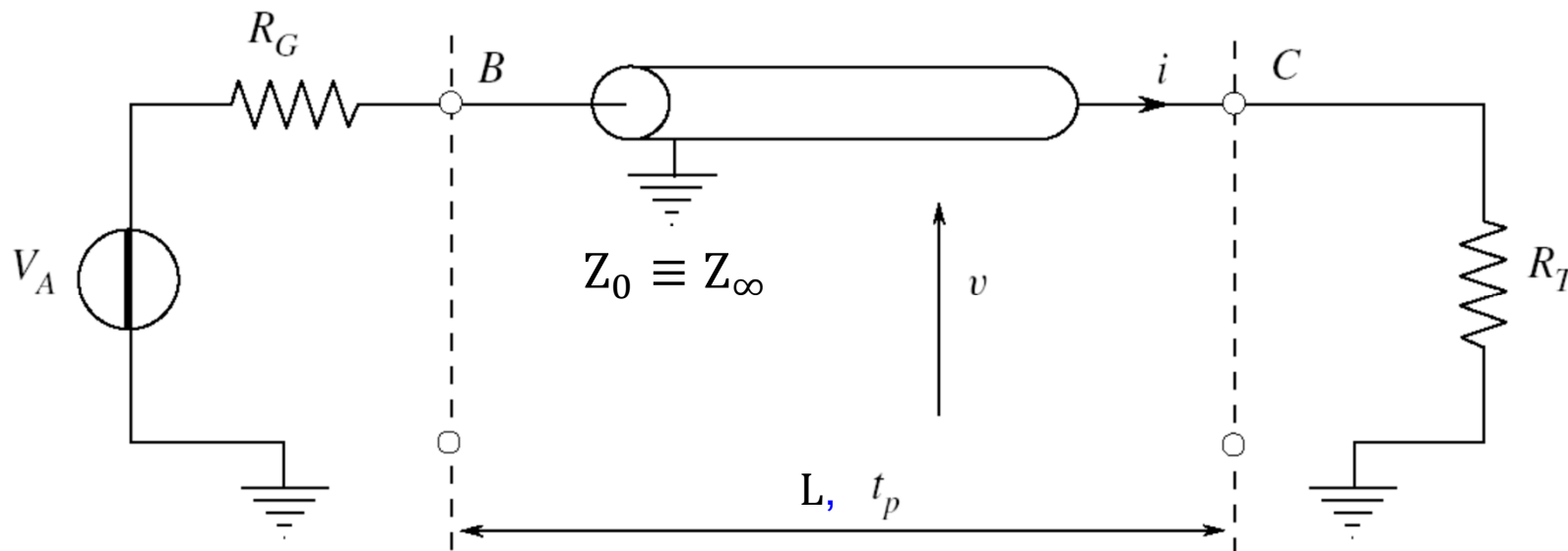- b) Repeat the calculation with $R_G = 270 \, \Omega$ and $R_G = 15 \, \Omega$



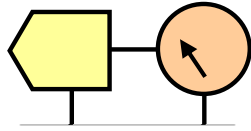

Problem 1a,b - Solution

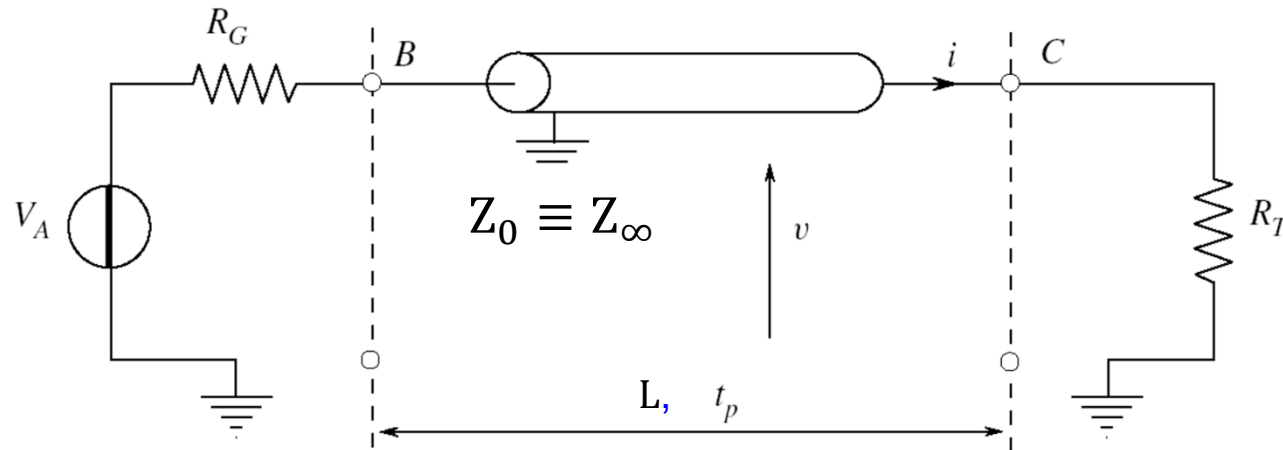


We first calculate the **reflection coefficients** $\Gamma_G \equiv \Gamma_B$ and $\Gamma_T \equiv \Gamma_C$ at the near and far-end respectively:

$$\Gamma_G = \frac{R_G - Z_\infty}{Z_\infty + R_G} = \begin{cases} 0, & \text{with } R_G = 50 \, \Omega \\ 0.69, & \text{with } R_G = 270 \, \Omega ; \\ -0.54, & \text{with } R_G = 15 \, \Omega \end{cases} \quad \Gamma_T = \frac{R_T - Z_\infty}{Z_\infty + R_T} = 1$$


Moreover $t_p = \frac{L}{U} = 0.8 \, \text{ns}$.


At the time instant $t = 0$ the **voltage at the near-end** is:

$$V_B(0) = \frac{Z_\infty}{Z_\infty + R_G} V_A = \begin{cases} 2.5 \, \text{V}, & \text{with } R_G = 50 \, \Omega \\ 0.8 \, \text{V}, & \text{with } R_G = 270 \, \Omega \\ 3.85 \, \text{V}, & \text{with } R_G = 15 \, \Omega \end{cases}$$

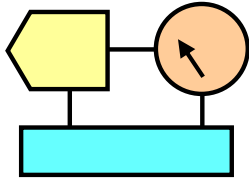


Problem 1 - Solution

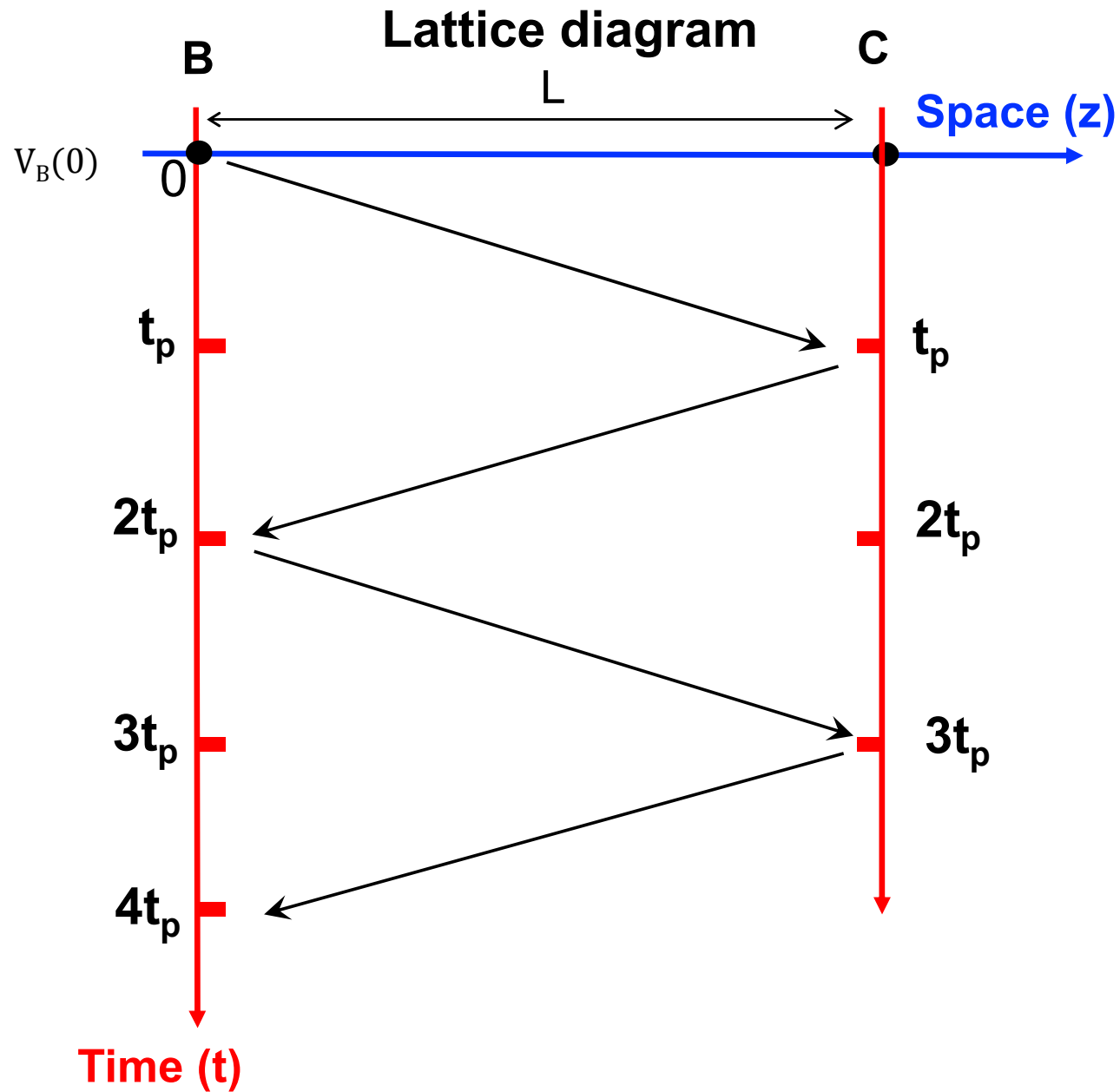


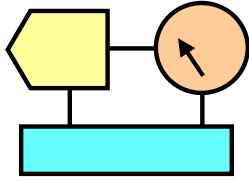


Problem 1 - Solution


Lattice diagram

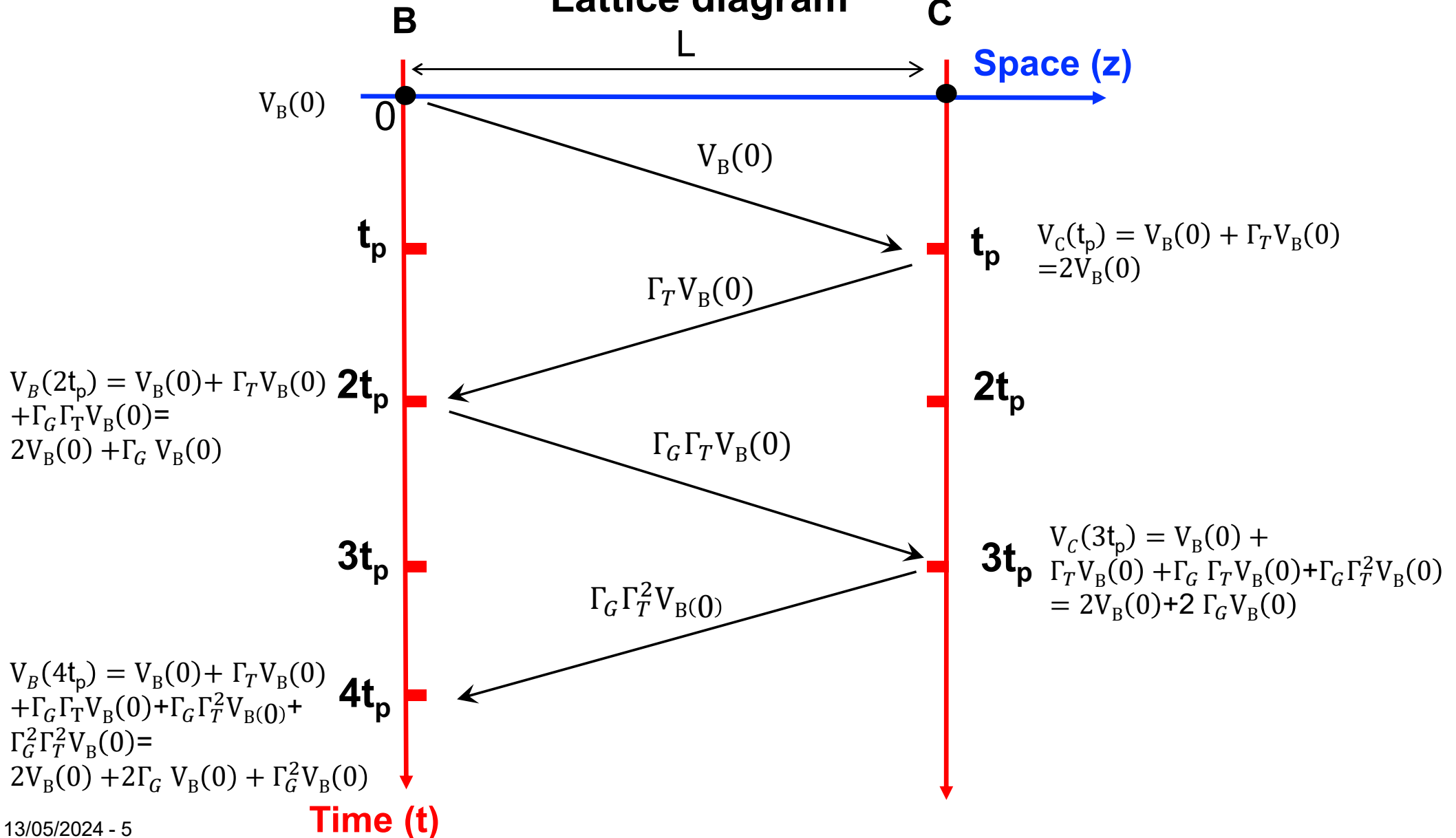

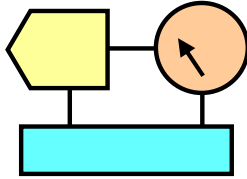

Problem 1a,b - Solution

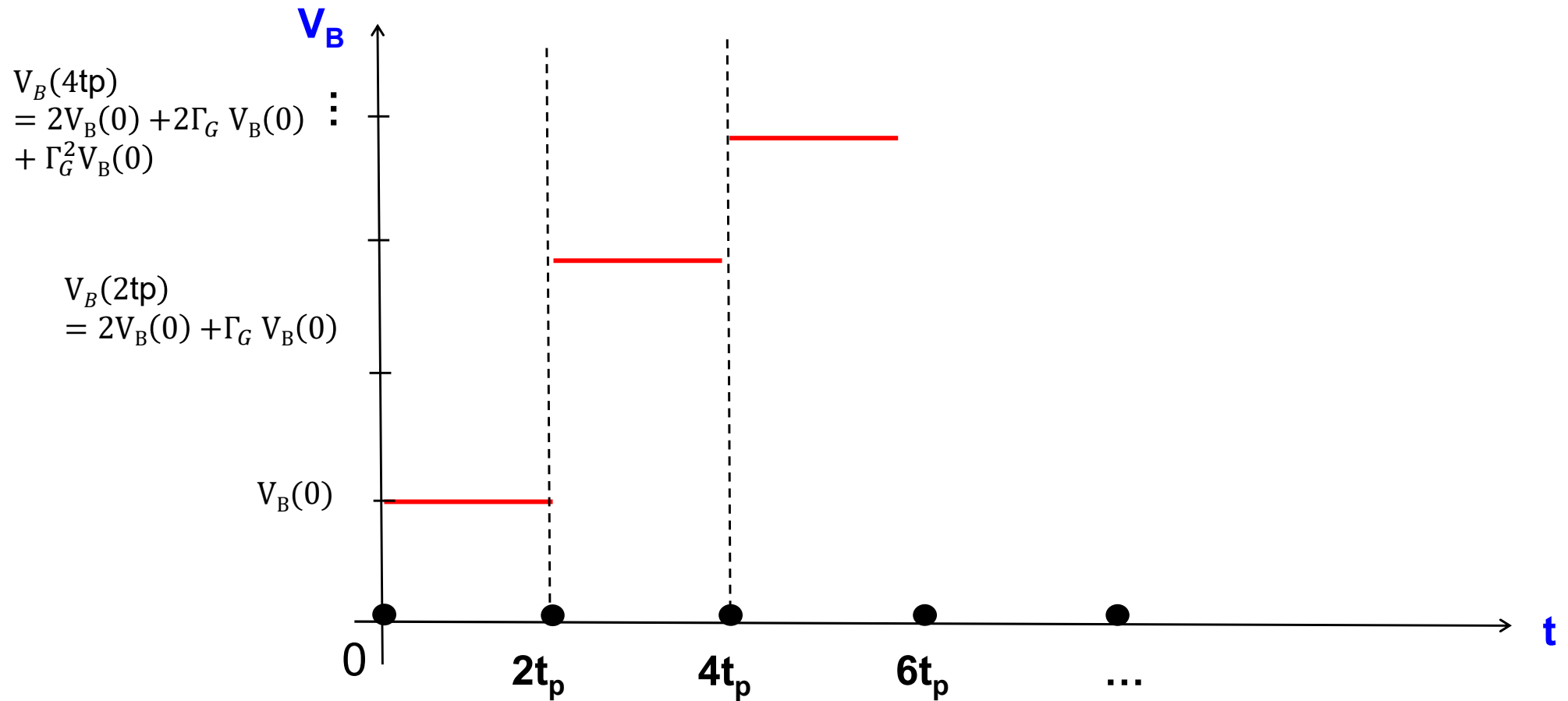


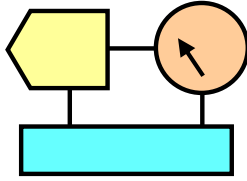


Problem 1a,b - Solution

Staircase behaviour

$$R_G = 270 \, \Omega$$

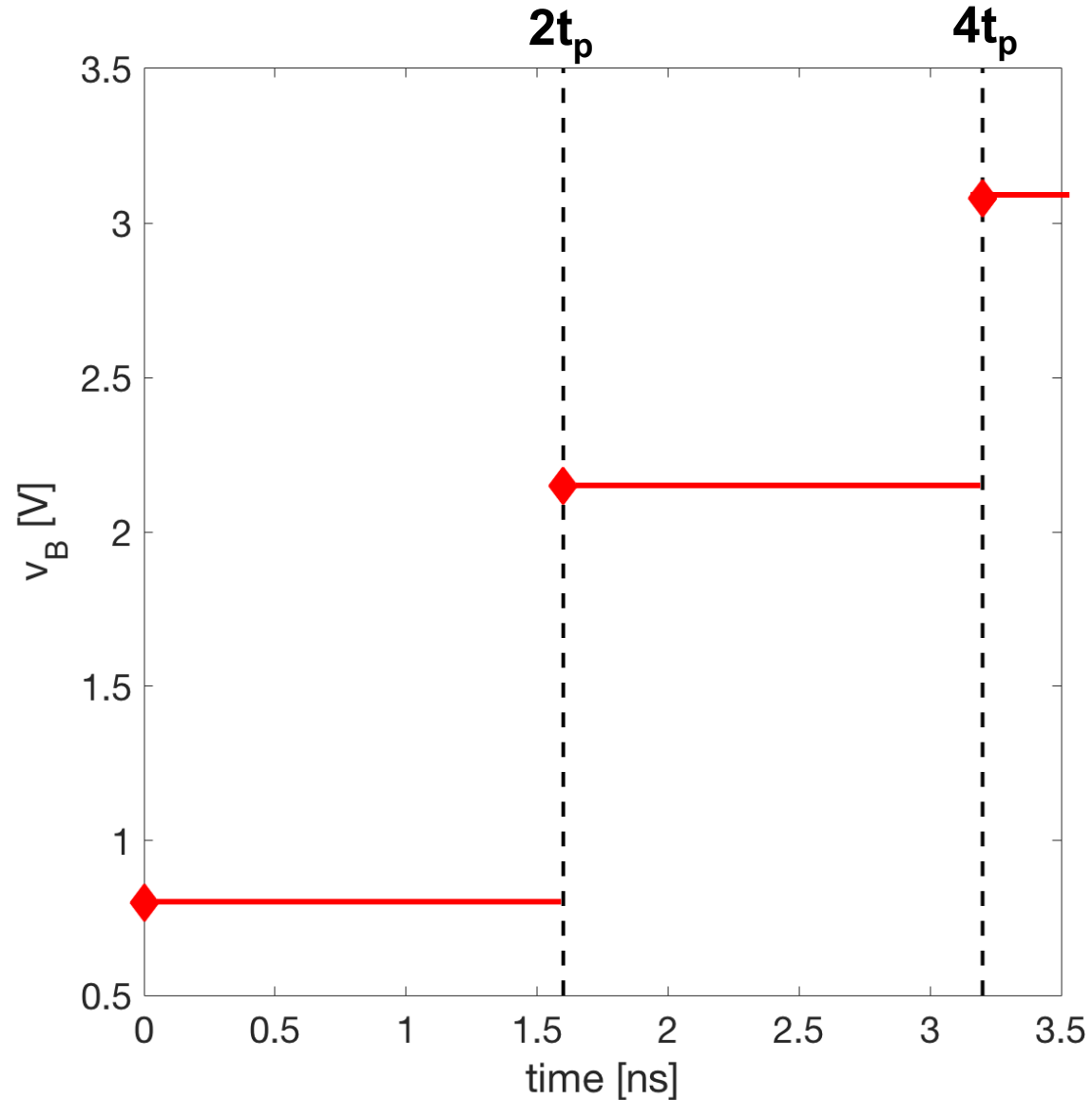

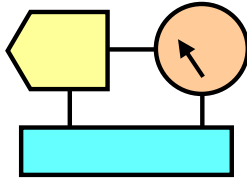



Problem 1a,b - Solution


Staircase behaviour

$$R_G = 270 \, \Omega$$

Note that at steady state the transmission line behaves as an equipotential wire. Thus for $\Gamma_T = 1$:

$$V_B(\infty) = V_C(\infty) = V_A$$

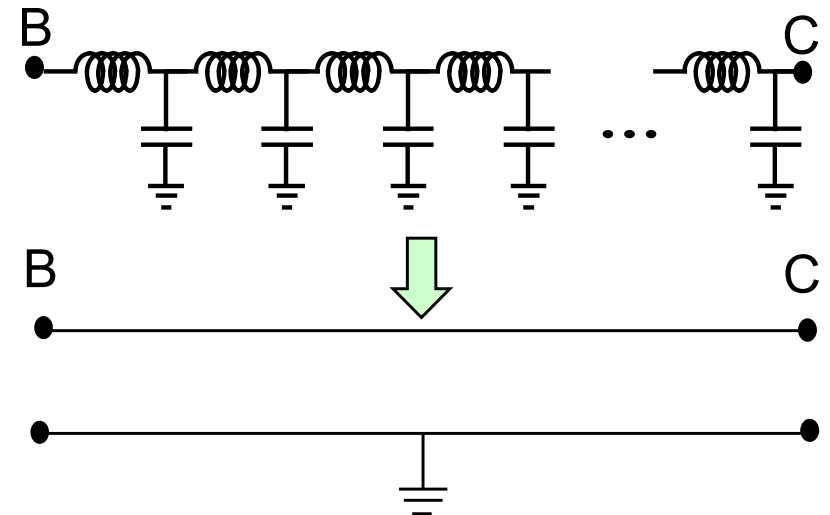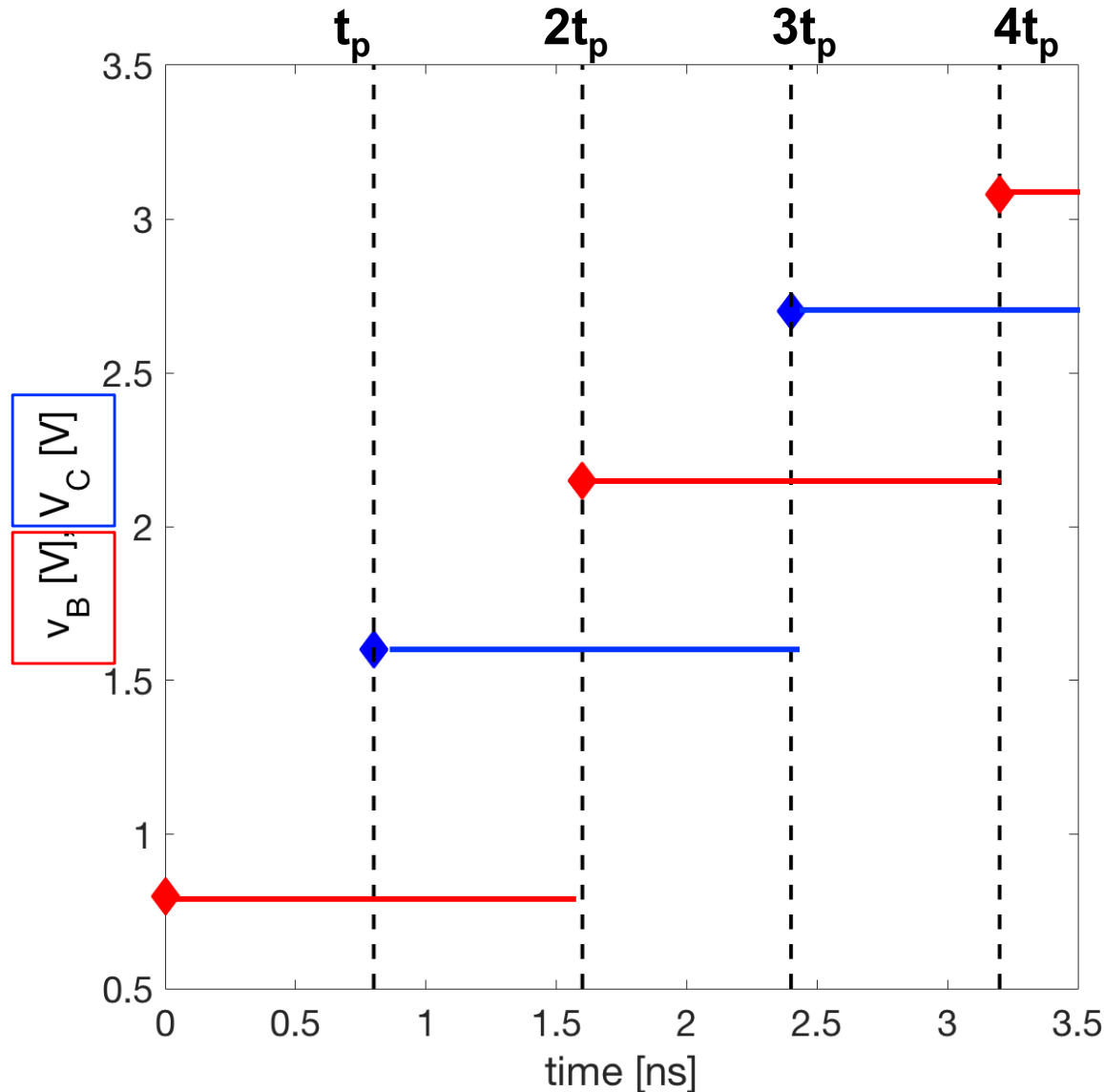

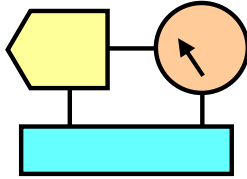

Problem 2 – Assignment

Incident Wave Switching


- a) Calculate the driver output resistance (R_O) for IWS driving for a connection with:

L \rightarrow H transition with $V_A = 0\text{ V} \rightarrow 4\text{ V}$

Receiver threshold $V_T = 2.5\text{ V}$

$Z_\infty = 70\ \Omega$ and open circuit termination

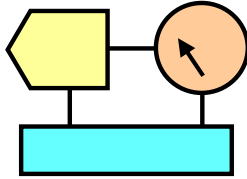- b) Explain why this configuration can give multiple transition for a receiver placed at the far-end. Indicate how multiple transitions can be eliminated
- c) Draw qualitatively the voltage $V_C(t)$ in the case a capacitor C_L is connected at the far end.



Problem 2a,b - Solution

Since **IWS** requires $V_B(0) > V_T$ for L→H transition and:

$$V_B(0) = \frac{Z_\infty}{Z_\infty + R_O} V_A$$


using the problem data, we get the following constraint on R_O :

$$R_O < Z_\infty \left(\frac{V_A}{V_T} - 1 \right) = 70 \, \Omega \left(\frac{4 \, \text{V}}{2.5 \, \text{V}} - 1 \right) = 42 \, \Omega$$

Since the reflection coefficient at the near-end (driver side) is given by:

$$\Gamma_B = \frac{R_O - Z_\infty}{Z_\infty + R_O} < 0$$


we get negative terms that sums up at the far-end (receiver side) that may cause the voltage at the far-end $V_C(t)$ to become smaller than V_T and in turn **multiple transitions**. Multiple transitions can be eliminated by matched far-end termination: $R_T = Z_\infty$.

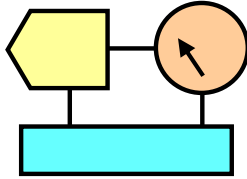

Problem 2c – Hint for solution

For a first approximation analysis, the far-end capacitor with a capacitance C_L can be considered a short circuit when the step arrives at the termination ($\Gamma_T = -1$), and an open circuit ($\Gamma_T = 1$) after the transient. Therefore at $t = t_p$ (for the far-end) and $t = 2t_p$ (for the near-end) the waveform corresponds to **short circuit** at the far-end. For $t \gg$ transient time associated to the capacitor charge the waveforms will correspond to an **open line**. During the transient at termination we expect an exponentially increasing voltage V_C .

NOTE: We will see an example of this behaviour during LAB2

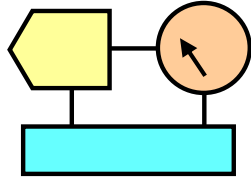


Problem 3 – Assignment

Transmission times and total skew time

Consider a backplane with $L_U = 8 \text{ nH/cm}$, $Z_\infty = 85 \Omega$ (without capacitive load), length $L = 48 \text{ cm}$, open circuit termination, and 24 connectors. Each board that can be inserted in the connectors has an input capacitance of 35 pF . The system can have from 2 to 24 connected boards.


Driver/receiver CMOS: $V_{DD} = 3.3 \text{ V}$; $R_O = 95 \Omega$; $V_{IH} = 2 \text{ V}$, $V_{IL} = 1 \text{ V}$.

- Calculate t_p in the cases of 2 and 24 connected boards.
- Calculate t_{TXmin} and t_{TXmax} for 2 connected boards in the two extremes of the line
- Calculate t_{TXmin} and t_{TXmax} with 24 connected boards
- Calculate the maximum R_{OH} to drive the line in IWS mode in the case of 24 inserted boards

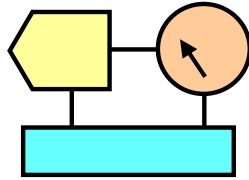

Problem 3a - Solution

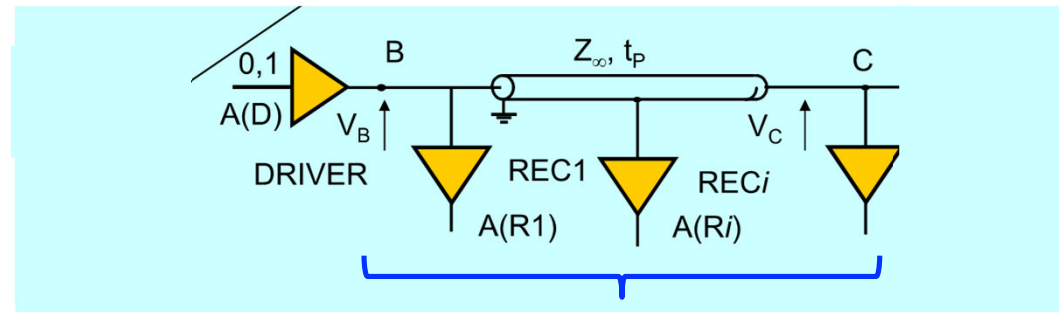a) Consider the following **Backplane scheme**:



Max 24 boards equally spaced

If consider **2 boards** connected to the transmission line and we assume that this configuration **does not load the line with a capacitance load**:


$$t_p = \frac{L}{U} \text{ where } U = \frac{1}{\sqrt{L_U C_U}} \text{ and } C_U = \frac{L_U}{Z_\infty^2}$$

Using the problem data:

$$C_U = \frac{8 \text{ nH/cm}}{(85 \Omega)^2} = 1.1 \text{ pF/cm}; U = \frac{1 \text{ cm}}{\sqrt{8 \text{ nH} \times 1.1 \text{ pF}}} = 0.11 \times 10^{11} \frac{\text{cm}}{\text{s}}$$

then:

$$t_p = \frac{48 \text{ cm}}{1.1 \times 10^{10} \frac{\text{cm}}{\text{s}}} = 4.4 \text{ ns}$$

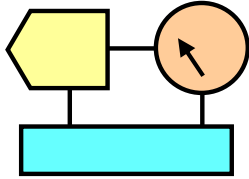

Problem 3a - Solution

In case of a number of boards $n > 2$ the total capacitance per unit length is:

$$C'_U = C_U + \frac{C_{in}}{L}$$

from which:


$$U' = \frac{1}{\sqrt{L_U C'_U}}; t'_p = \frac{L}{U'}$$

Using the problem data:

$$\begin{aligned} C'_U &= \frac{8 \text{ nH/cm}}{(85 \Omega)^2} + \frac{35 \text{ pF} \times 24}{48 \text{ cm}} = 18.6 \frac{\text{pF}}{\text{cm}}; U' = \frac{1 \text{ cm}}{\sqrt{8 \text{ nH} \times 18.6 \text{ pF}}} \\ &= 0.026 \times 10^{11} \frac{\text{cm}}{\text{s}} \end{aligned}$$

then:

$$t'_p = \frac{48 \text{ cm}}{0.026 \times 10^{11} \frac{\text{cm}}{\text{s}}} = 18.46 \text{ ns}$$

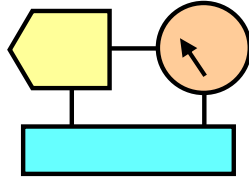

Problem 3b - Solution

b) In presence of **2 connected boards at the extremes** of the line in order to determine t_{TXmax} and t_{TXmin} for $L \rightarrow H$ transition we consider that the voltage at the near-end and far-end at multiple of t_p . At near-end we have:

$$V_B(0) = \frac{Z_\infty}{Z_\infty + R_O} V_{DD} = \frac{85 \Omega}{85 \Omega + 95 \Omega} 3.3 V = 1.4 V > V_{IL} \Rightarrow t_{TXmin,B} = 0$$

$$V_B(2t_p) = V_B(0) + \Gamma_C V_B(0) + \Gamma_B \Gamma_C V_B(0) = 3.2 V > V_{IH} \Rightarrow t_{TXmax,B} = 2t_p$$

where we used:


$$\Gamma_B = \frac{R_O - Z_\infty}{Z_\infty + R_O} = \frac{95 \Omega - 85 \Omega}{85 \Omega + 95 \Omega} = 0.06; \Gamma_C = \frac{+\infty - Z_\infty}{Z_\infty + \infty} = 1 \text{ (open circuit)}$$

The voltage at the far-end is:

$$V_C(t_p) = 2V_B(0) = 2.8 V > V_{IH} \Rightarrow t_{TXmax,C} = t_p$$

Finally the total **skew time** is:

$$t_k = t_{TXmax} - t_{TXmin} = 2t_p = 2 \times 4.4 \text{ ns} = 8.8 \text{ ns}$$

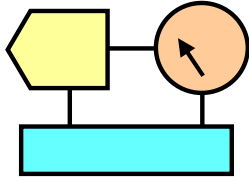


Problem 3c - Solution

c) In presence of **24 boards** we have:

$$Z'_{\infty} = \sqrt{\frac{L_U}{C'_U}} = \sqrt{\frac{L_U}{C_U}} \sqrt{\frac{1}{\left(1 + \frac{nC_i}{C_UL}\right)}} = \frac{Z_{\infty}}{4.1} = 20.7 \, \Omega; \quad \Gamma'_B = \frac{R_O - Z'_{\infty}}{Z'_{\infty} + R_O} = \frac{95 \, \Omega - 20.7 \, \Omega}{20.7 \, \Omega + 95 \, \Omega} = 0.64$$

In order to determine t_{TXmax} and t_{TXmin} we calculate the voltage at the near-end and far-end at multiple of $t'_p = 18.46 \, ns$ that we have calculated at point a):

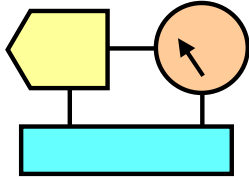

Problem 3c - Solution

c) In presence of **24 boards** we have:

$$Z'_{\infty} = \sqrt{\frac{L_U}{C'_U}} = \sqrt{\frac{L_U}{C_U}} \sqrt{\frac{1}{\left(1 + \frac{nC_i}{C_UL}\right)}} = \frac{Z_{\infty}}{4.1} = 20.7 \, \Omega; \quad \Gamma'_B = \frac{R_O - Z'_{\infty}}{Z'_{\infty} + R_O} = \frac{95 \, \Omega - 20.7 \, \Omega}{20.7 \, \Omega + 95 \, \Omega}$$

$$= 0.64$$

In order to determine t_{TXmax} and t_{TXmin} we calculate the voltage at the near-end and far-end at multiple of $t'_p = 18.46 \, ns$ that we have calculated at point a):


$$V_B(0) = \frac{Z'_{\infty}}{Z'_{\infty} + R_O} V_{DD} = \frac{20.7 \, \Omega}{20.7 \, \Omega + 95 \, \Omega} 3.3 \, V = 0.6 \, V < V_{IL} \Rightarrow \text{no switch}$$

$$V_C(t'_p) = V_B(0) + \Gamma_C V_B(0) = 1.2 \, V > V_{IL} \Rightarrow t_{TXmin,C} = t'_p = \mathbf{18.46 \, ns}$$

$$V_B(2t'_p) = V_B(0) + \Gamma_C V_B(0) + \Gamma'_B \Gamma_C V_B(0) = 1.58 \, V < V_{IH}, 1.58 \, V > V_{IL}$$

$$\Rightarrow t_{TXmin,B} = \mathbf{2t'_p}$$

$$V_C(3t'_p) = V_B(0) + \Gamma_C V_B(0) + \Gamma'_B \Gamma_C V_B(0) + \Gamma_C \Gamma_C \Gamma'_B V_B(0) = 1.97 \, V < V_{IH}$$

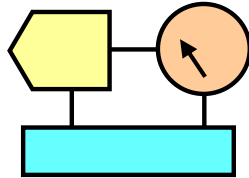

Problem 3d - Solution

Analogously:

$$V_B(4t'_p) = V_B(0) + \Gamma_C V_B(0) + \Gamma'_B \Gamma_C V_B(0) + \Gamma_C^2 \Gamma'_B V_B(0) + \Gamma_C^2 \Gamma_B'^2 V_B(0) = 2.21 \text{ V} > V_{IH}$$

$$\Rightarrow t_{TXmax,B} = 4t'_p$$

$$V_C(5t'_p) = V_B(0) + \Gamma_C V_B(0) + \Gamma'_B \Gamma_C V_B(0) + \Gamma_C^2 \Gamma'_B V_B(0) + \Gamma_C^2 \Gamma'_B \Gamma'_B V_B(0) + \Gamma_C^3 \Gamma'_B \Gamma'_B V_B(0)$$

$$= 2.45 \text{ V} > V_{IH} \Rightarrow t_{TXmax,C} = 5t'_p = 5 \times 18.46 \text{ ns} = 92.3 \text{ ns}$$

Finally, the total **skew time** is $t_k = t_{TXmax} - t_{TXmin} = 4t'_p = 4 \times 18.46 \text{ ns} = 73.84 \text{ ns}$

Note that all the intermediate receivers have $t_{TXmin,i} > t_{TXmin,C}$ (since $t_{TXmin,B} > t_{TXmin,C}$) and $t_{TXmax,i} < t_{TXmax,C}$ (since $t_{TXmax,B} < t_{TXmax,C}$).


d) In the case of **24 inserted boards** we have:

$$V_B(0) = \frac{Z'_\infty}{Z_\infty + R_{OH}} V_{DD} = \frac{20.7 \Omega}{20.7 \Omega + R_{OH}} 3.3 \text{ V}$$

Hence the values of R_{OH} that **drive a IWS** are given by the following relation:

$$\frac{20.7 \Omega}{20.7 \Omega + R_{OH}} 3.3 \text{ V} > V_{IH} = 2 \text{ V}$$

Then their maximum value is:

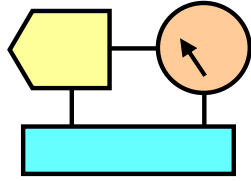


Problem 4 - Assignment

A track on a PCB backplane has characteristic impedance $Z_0 = 95 \, \Omega$ (with no load), wave propagation speed $U = 0.65 \, c$. The track length is $L = 30 \, \text{cm}$, without terminations, and 15 equally spaced devices are connected to the track. The total capacitive load of these devices increases the distributed track capacitance (towards GND) by a factor 20 (loaded unity capacitance = unloaded capacitance \times 20).


The interface uses CMOS circuits, with power supply $5 \, \text{V}$, and the following parameters: $V_{OH} = 4 \, \text{V}$, $I_{OH} = -16 \, \text{mA}$, $V_{OL} = 0.8 \, \text{V}$, $I_{OL} = 16 \, \text{mA}$, $V_{IH} = 2.7 \, \text{V}$, $V_{IL} = 1.3 \, \text{V}$.

Further assumptions: the PCB tracks can be considered lossless transmission lines, and linear equivalent circuits can be used for drivers and receivers.

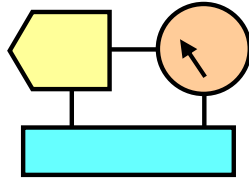


Problem 4 - Assignment

- Find the characteristic impedance Z'_0 and the propagation speed U' of the loaded track, and evaluate the propagation time t_p over the full length of the connection, for a fully loaded track.
(propagation speed $U = 1/\sqrt{L_U C_U}$)
- Find the equivalent output resistance of drivers, for H and L states (respectively R_{OH} and R_{OL}), and find the minimum and maximum transmission times t_{TXmin} and t_{TXmax} from a driver placed at one end and a receiver placed at any position along the connection, for fully loaded track without termination in case of L→H transition.
- Evaluate the equivalent driver output resistance R'_{OH} required to operate a receiver connected at any intermediate point of the track in IWS (Incident Wave Switching) for the L → H transition, with $NM = 100$ mV, and line driven from one end.
Using drivers with equivalent output resistance R'_{OH} , what should be connected at the opposite end to guarantee correct operation?

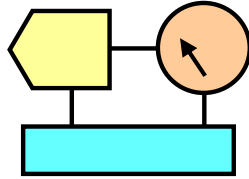

Problem 4 - Assignment

- d) Draw the Information and Control signals (INF, STB) at Driver and at Receiver, and the destination register clock CK for a **synchronous** write cycle and evaluate cycle duration with the following parameters.
- Interconnection: $t_K = 25 \text{ ns}$, $t_{TXmin} = 20 \text{ ns}$
 - Receiver register: $t_{SU} = 10 \text{ ns}$, $t_H = 5 \text{ ns}$
- e) Draw the Information and Control signals (INF, STB, ACK) at Driver and at Receiver, and the destination register clock CK for an **asynchronous** transfer cycle and evaluate cycle duration with the following parameters.
- Interconnection: $t_K = 25 \text{ ns}$, $t_{TXmin} = 20 \text{ ns}$
 - Receiver register: $t_{SU} = 10 \text{ ns}$, $t_H = 5 \text{ ns}$

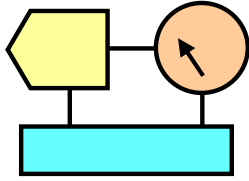

Problem 4a - Solution

a) We first observe that:

$$U = 0.65 c = 0.65 \times 3 \times 10^8 \frac{\text{m}}{\text{s}} = 0.65 \times 3 \times 10^8 \times 10^2 \times 10^{-9} \frac{\text{cm}}{\text{ns}} = 19.5 \frac{\text{cm}}{\text{ns}}$$

From the definition of the **characteristic impedance**, denoting with $C'_U = 20C_U$ the loaded unity capacitance, in case of loaded track:


$$Z'_0 \equiv Z'_\infty = \sqrt{\frac{L_U}{C'_U}} = \sqrt{\frac{1}{20}} \sqrt{\frac{L_U}{C_U}} = \sqrt{\frac{1}{20}} Z_0 = 21.24 \Omega$$

Analogously from the definition of the **propagation speed**, in case of loaded track:

$$U' = \sqrt{\frac{1}{L_U C'_U}} = \sqrt{\frac{1}{20}} \sqrt{\frac{1}{L_U C_U}} = \sqrt{\frac{1}{20}} U = 4.36 \frac{\text{cm}}{\text{ns}}$$

Thus in case of fully loaded track the **propagation time** t_p is:

$$t_p = \frac{L}{U'} = \frac{30 \text{ cm}}{4.36 \text{ cm/ns}} = 6.88 \text{ ns}$$

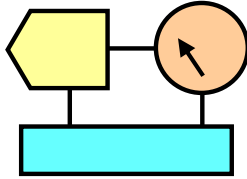

Problem 4b - Solution

b) The equivalent **output resistances of drivers**, for H and L states are given by:

High State

$$V_O = V_{DD} + I_{OH}R_{OH} \Rightarrow$$

$$R_{OH} = \frac{V_{DD} - V_{OH}}{-I_{OH}} = \frac{5 \text{ V} - 4 \text{ V}}{16 \text{ mA}} = 62.5 \Omega$$

Low State

$$V_O = R_{OL}I_O \Rightarrow$$


$$R_{OL} = \frac{V_{OL}}{I_{OL}} = \frac{0.8 \text{ V}}{16 \text{ mA}} = 50 \Omega$$

We use the previous results to calculate the voltage V_B at the driver-end for $L \rightarrow H$ transition at the initial time $t = 0$:

$$V_B(0) = \frac{Z'_0}{Z'_0 + R_{OH}} V_{DD} = \frac{21.24 \Omega}{21.24 \Omega + 62.5 \Omega} \times 5 \text{ V} = 1.27 \text{ V}$$


The reflection coefficients at the driver or near-end and at the line termination are respectively:


$$\Gamma'_B = \frac{R_{OH} - Z'_0}{Z'_0 + R_{OH}} = \frac{62.5 \Omega - 21.24 \Omega}{62.5 \Omega + 21.24 \Omega} = 0.49; \Gamma_T = 1$$

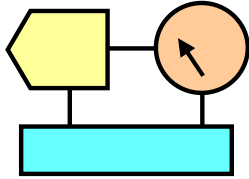

Problem 4b - Solution

Using linear models and with the help of the **lattice diagram** we can evaluate the voltages at **driver**, at **termination**, and **along the line**.

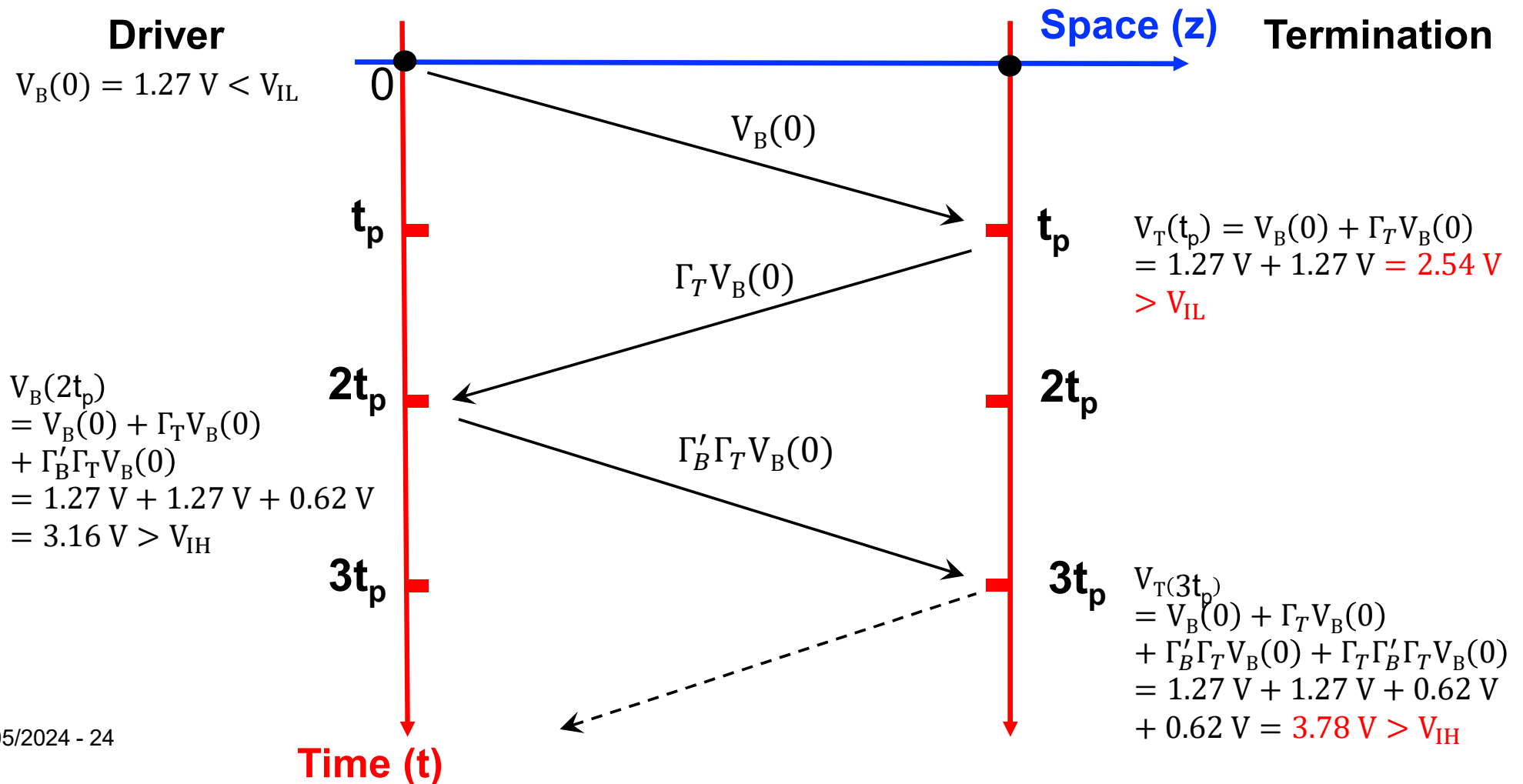


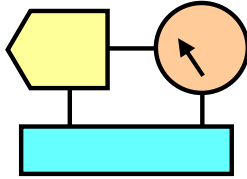

Problem 4b - Solution

The following table describes what happens on the interconnection over time:

time	Voltage at driver (V)	Travelling wave (V)	Direction	Voltage at termination (V)	Remarks
0	1,27				First step does not cross V_{il}
		1,27	$D \rightarrow T$		First step travelling towards Termination
t_p				$1,27 + 1,27 = 2,54$	First step reflected from Term. First step + refl crosses V_{il} at Term. : $T_{xmin} = T_p$
		1,27	$D \leftarrow T$		First reflection travels to Driver
$2t_p$	$1,27 + 1,27 + 0,62 = 3,16$				Reflected wave at driver; V_{ih} crossed for RX at Driver
		0,62	$D \rightarrow T$		Second reflect. towards Term
$3t_p$				$2,54 + 0,62 + 0,62 = 3,78$	V_{ih} crossed for RX at Term $T_{xmax} = 3 T_p$ All RX switched, not worth to continue further the analysis

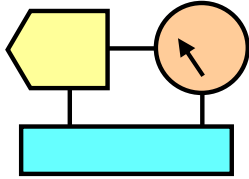

Problem 4b - Solution

Hence the **minimum** and **maximum propagation times** for a receiver at the **termination** are given by:


$$t_{TX\min} = 6.88 \text{ ns} \text{ and } t_{TX\max} = 3 \times 6.88 \text{ ns} = 20.64 \text{ ns}$$

and thus we have the **skew time**:

$$t_k = t_{TX\max} - t_{TX\min} = 13.76 \text{ ns}$$

This also corresponds to the maximum skew time of any intermediate receiver.

Note: For $H \rightarrow L$ transition, the value of R_{OL} is different, therefore also the first step amplitude and the reflection coefficient at the driver-end are different. All wave amplitudes must be evaluated with the new data.

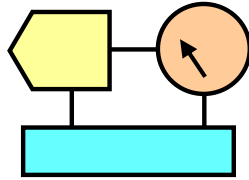

Problem 4c - Solution

c) In order to have IWS at near-end point of the track the first step must be higher than:

$$V_{IH} + NM = 2.7 \text{ V} + 0.1 \text{ V} = 2.8 \text{ V}$$


Hence R'_{OH} must satisfy the relation:

$$2.8 \text{ V} = \frac{Z'_0}{Z'_0 + R'_{OH}} V_{DD} = \frac{21.24 \Omega}{21.24 \Omega + R'_{OH}} 5 \text{ V}$$

From which we obtain: $R'_{OH} = 16.7 \Omega$

This value of R'_{OH} is lower than Z'_0 , and causes negative reflection coefficient at driver, with oscillating waveforms on the line, and possible multiple crossing of thresholds. Reflections at far end must be avoided by placing a matched termination resistor, or at least reduced with a “almost matched” termination. Note that a driver at intermediate position is loaded by two Z'_0 lines in parallel (left and right branch); the output resistance R''_{OH} must be lower than R'_{OH} in order to have IWS. Hence, in this case we get:


$$2.8 \text{ V} = \frac{Z'_0/2}{Z'_0/2 + R''_{OH}} V_{DD} = \frac{10.62 \Omega}{10.62 \Omega + R''_{OH}} 5 \text{ V} \Rightarrow R''_{OH} = 8.3 \Omega$$

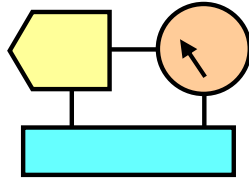

Problem 4d - Solution

d) Timing diagram


At Source

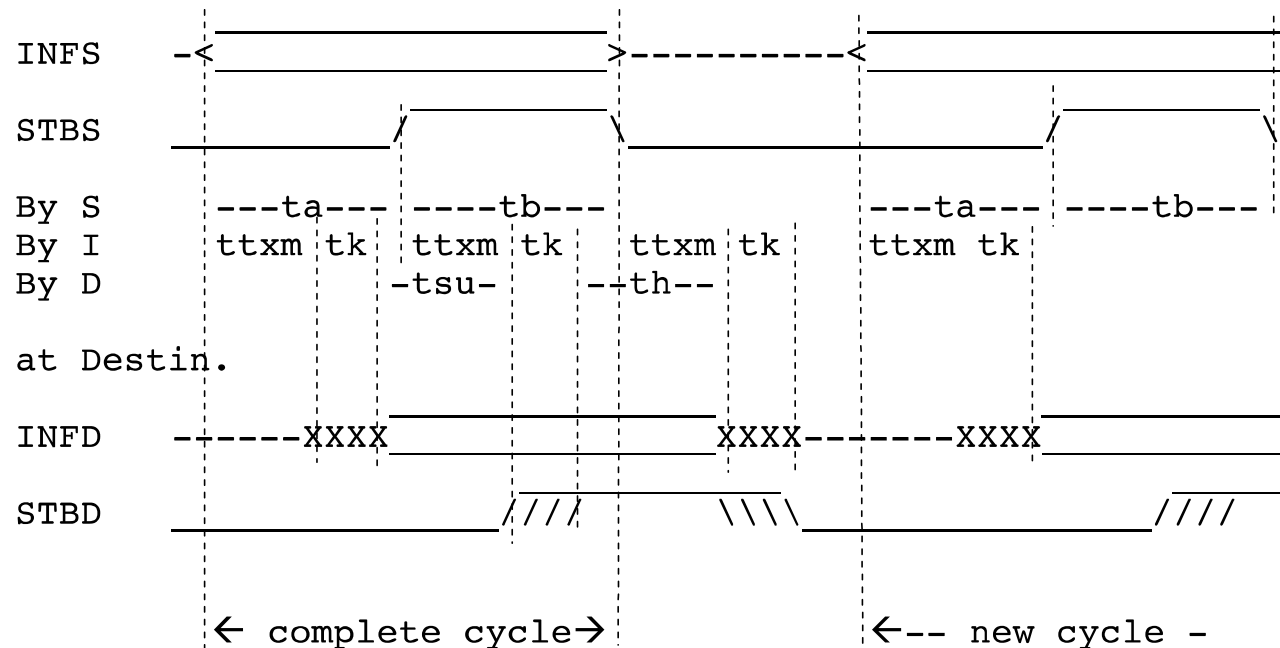

The **total cycle time** is:


$$T_{WR} = t_A + t_B = 2 \times t_K + t_H + t_{SU} = 65 \text{ ns}$$

We observe that the clock CK for the destination register is the Strobe signal STB (at destination). Total cycle time is independent from t_{TXmin} , and related only with t_K , t_{SU} , and t_H .

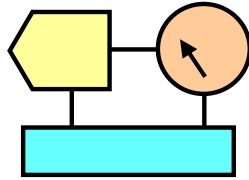

Problem 4e - Solution

e) Timing diagram

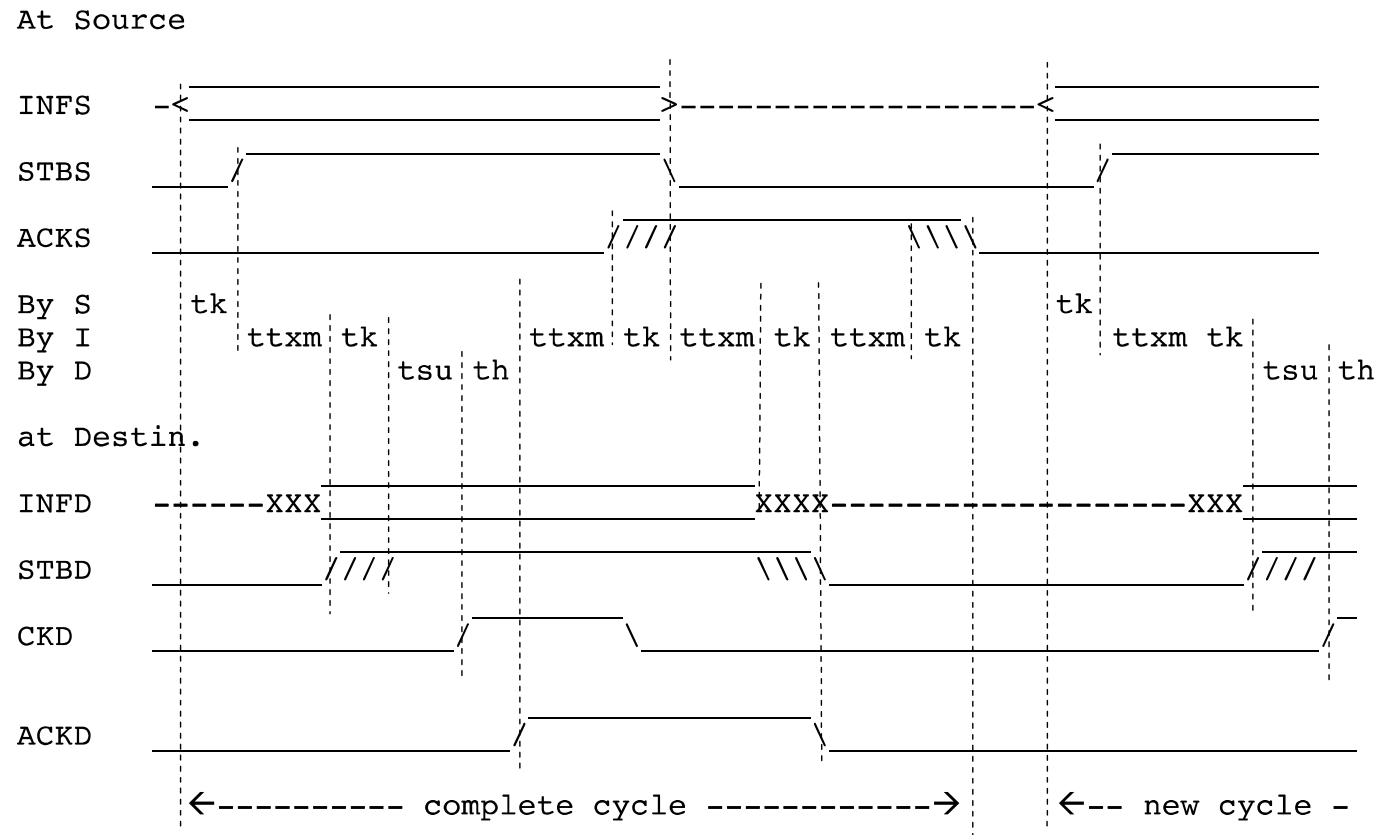

The **total cycle time** is in the worst case ($t_{TX} = t_{TXmin} + t_k$):

$$T_{WR} = 4 \times (t_K + t_{TXmin}) + t_K + t_H + t_{SU} = 220 \text{ ns}$$

We observe that the CK for the destination register is CKD, generated by the **destination interface circuit**.