

Surname
Name
ID

COMPITO "ENG"

Room

Part A – Quiz

(Report with X the correct answer in the table – Do not write in the row "Total points")

Quiz	A1	A2	A3	A4	A5	A6	A7	A8	A9	A10
Answer a										
Answer b										
Answer c										
Answer d										
Total points										

Quiz A1

Consider a 8 bit A/D conversion system. By adding two more bits, the signal to noise ratio due to quantization

- a) decreases of 6 dB
c) increases of 1.76 dB

- b) increases of 6 dB
d) increases of 12 dB

$$SNR_q = 6N + 1.76 \text{ dB}$$

$$SNR_q = 6(N+2) + 1.76 \text{ dB} = 6N + 12 + 1.76 \text{ dB}$$

Quiz A.2

Consider a square wave generator realized with Schmitt trigger inverter, one resistor and one capacitor. The voltage out of the Schmitt trigger inverter is:

- a) exponential b) square wave c) linear d) sine wave



Quiz A.3

Consider a synchronous write cycle; the delay, at source, between INF and STB signal is:

- a) $T_{su} + T_k$ b) T_k c) T_h d) $T_k + T_{txmin}$

Quiz A.4

Consider a voltage step propagating in a transmission line with open circuit termination, $R_0 = Z_\infty$ and $V_{DD} = 2V$. The first incident voltage step is:

- a) 1 V b) 2 V c) 0.5 V d) 1.5 V

$$V_B(\infty) = \frac{Z_0}{R_0 + Z_0} V_{DD} = \frac{R_0}{R_0 + R_0} V_{DD} = V_{DD}/2$$

Quiz A.5

Series voltage regulators: the efficiency is:

- a) 1 b) >1 c) <1 d) 100

Quiz A.6

How many voltage comparators are required in a 4 bit FLASH ADC?

- a) 1 b) 15 c) 4 d) 8

$$\Rightarrow \text{comparators} = 2^N - 1 = 2^4 - 1 = 15$$

Quiz A.7

If we reduce of a factor of 2 the voltage supply V_{DD} of a CMOS logic gate, then the dynamic power consumption:

- A) increases of factor 2 b) reduces of factor 1/2
c) increases of factor 4 d) reduces of factor 1/4

$$P_{DD} = \frac{V_{DD}^2}{2} C_L f$$

Quiz A.8

A flash memory cell consists in:

- a) one FAMOS
- b) one FAMOS and one capacitor C_s
- c) 1 MOS and one capacitor C_s
- d) one NMOS, one PMOS and two capacitors

Quiz A.9

A FPGA logic block contains:

- a) Look-Up Tables and several AND/OR gates
- b) several AND/OR gates and several flip-flops
- c) Look-up Table and several flip-flops
- d) programmable switch only

Quiz A.10

The output of a CAM memory is:


- a) a control signal
- b) a data
- c) a command
- d) an address

Parte B – Problem B.1

Consider 4 analog sinusoidal signals with voltage in the range between -4V and +4V. The signals are converted with an A/D conversion system using only one S/H and one ADC. The S/H acquisition time is 800ns. The ADC is a 8 bit successive approximation converter with clock frequency of 60 MHz and input dynamics from -5V to +5V. The signals are sampled with over-sampling factor $K=3.5$.

- a) Plot the block diagram of the A/D conversion system. Indicate if the conditioning amplifier is required; trace the characteristic (ie: V_{out} versus V_{in}) of the conditioning amplifier and plot a circuit of this conditioning amplifier.

Block diagram: see slide of lecture

 

- b) Calculate the maximum possible input frequency of each input signal and calculate the signal to noise ratio due to quantization.

$$T_{s_{min}} \approx T_c + T_{S/H} + T_{mux} = NT_c + T_{S/H} = 800 \text{ ns} + 8/60 \text{ MHz} = 933 \text{ ns}$$

$$f_{S/H_{max}} \approx 1 \text{ MHz}$$

$$f_{signal_{max}} = 2B_{max} \cdot K = \frac{1 \text{ MHz}}{4}$$

$$B_{max} = 35.7 \text{ kHz}$$

Part B – Problem B.2

One driver with voltage supply equal to 3,3 V ($V_{OH}=3.3V$, $V_{OL}=0V$) is used for driving a transmission line with $Z_0 = 60 \Omega$, propagation speed $U = 0,6$ c, length 25 cm and termination $R_T=100 \Omega$. The receivers are CMOS circuits with $V_{IL} = 1V$, $V_{IH} = 2,2$ V. Consider L-H transition and answer to the following questions:

a) Calculate the value of the driver output resistance R_0 to have RWS on the first reflected wave.

We must avoid IWS and satisfy RWS:

$$\rightarrow \text{no IWS} \Rightarrow V_B(0) < V_{IH} \Rightarrow \frac{Z_0 \cdot V_{DD}}{Z_0 + R_0} < V_{IH} \quad \boxed{R_0 > 30 \Omega}$$

$$\tau_T = \frac{R_T - Z_0}{R_T + Z_0} = 0.25$$


\rightarrow Switch on RWS \Rightarrow

$$\left. \begin{aligned} V_c(t_p) &= V_B(0) [1 + \tau_T] > V_{IH} \\ V_c(>t_p) &= V_B(0) [1 + \tau_T] > V_{IH} \end{aligned} \right\} \begin{aligned} 1.25 V_B(0) &> V_{IH} \\ \boxed{R_0 < 52.5 \Omega} \end{aligned}$$

b) Assuming now the far-end is open circuit, calculate:

- the steady state far-end voltage when the transient is concluded
- the maximum and minimum transmission time and the skew for a receiver connected to the far-end.

$$V_c(t \rightarrow \infty) =$$

 


$$V_c = \frac{R_T}{R_0 + R_T} V_{DD} = 2V$$

$$\text{with } R_0 = 40 \Omega$$

$$T_{TXmin} = t_p = T_{TXmax} \quad \text{because } V_c(t_p) = V_{DD} \cdot 0.6 \cdot 2 > V_{IH}$$

$$t_p = \frac{L}{U} = \frac{25 \text{ cm}}{0.6 \text{ c}} = 0.13 \cdot 10^{-8} \text{ s} = 1.3 \text{ ns}$$


Part B – Problem B.3

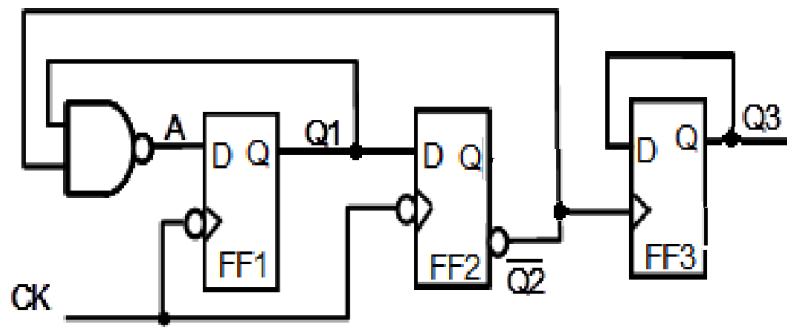

Consider the sequential circuit shown in the figure. All outputs Q are initially reset to zero.

 - a) Plot the timing diagrams of the outputs Q1, Q2*, A and Q3 for 5 CK cycles; assuming the following delays:

FF1, FF2 and FF3: $T_{ck \rightarrow Q} = 2 \text{ ns}$; $T_h = 1 \text{ ns}$; $T_{su} = 3 \text{ ns}$
NAND: $T_p = 5 \text{ ns}$ per H-L e 4 ns per L-H



- b) Calculate the maximum CK frequency when the components have the dynamic parameters of point (1)

$$T_{CK_{min}} = T_{CK \rightarrow Q}^{FF_2} + T_{NAND} + T_{su}^{FF_1} = 10 \text{ ns}$$

$$f_{CK_{max}} = 100 \text{ MHz}$$

- c) If $T_{ck} = 10 \text{ ns}$ specify if any FF will enter in metastable state.

Enter in unstable state

Part-B –Problem B.4

A DRAM memory has:

- 12 bit address, 4 bits are for column address and 8 bits are for row address.
- 8 bit words
- pass transistors with $C_d = 0.5 \text{ fF}$

The

a) Calculate the number of Word lines

$$\uparrow 2^8 = 256$$

b) Calculate the total number of memory cells

$$2^8 \times 2^4 \times 8 = 32768$$

$\uparrow 32 \text{ kbit}$

c) Calculate the capacitance of the bit line C_{BL}

$$C_{BL} = \# \text{ rows} \cdot C_d = 128 \text{ fF}$$

how much is femto ?