 


# APPLIED ELECTRONICS


## Class exercises with solutions



# APPLIED ELECTRONICS

 Part B:

- ☐ CMOS logic gate Static and Dynamic parameters
- ☐ Combinational logic circuits
- ☐ Sequential logic circuits and timing diagrams



# Problem 1- Assignment

## Static parameters

## Voltage compatibility

a) Consider a logic gate with the following static electrical parameters:


A } Output electrical parameters


$$V_{OL} = 0.37 \text{ V}, V_{OH} = 3.76 \text{ V}$$

B } Input electrical parameters

$$V_{IL} = 0.9 \text{ V}, V_{IH} = 3.15 \text{ V}$$

and check the voltage compatibility

 

 


# Problem 1

## Theoretical remind


### Input/output electrical parameters


- $V_{IH}$ : maximum value of the threshold  $V_T$ 
  - Input voltages  $V_I > V_{IH}$  are interpreted as H state
- $V_{IL}$ : minimum value of the threshold  $V_T$ 
  - Input voltages  $V_I < V_{IL}$  are interpreted as L state
- $V_{OH}$ : high state minimum output voltage
  - State H:  $V_O > V_{OH}$ , (as long as  $|I_O| < |I_{OH}|$ )
- $V_{OL}$ : low state maximum output voltage
  - State L:  $V_O < V_{OL}$ , (as long as  $|I_O| < |I_{OL}|$ )

 
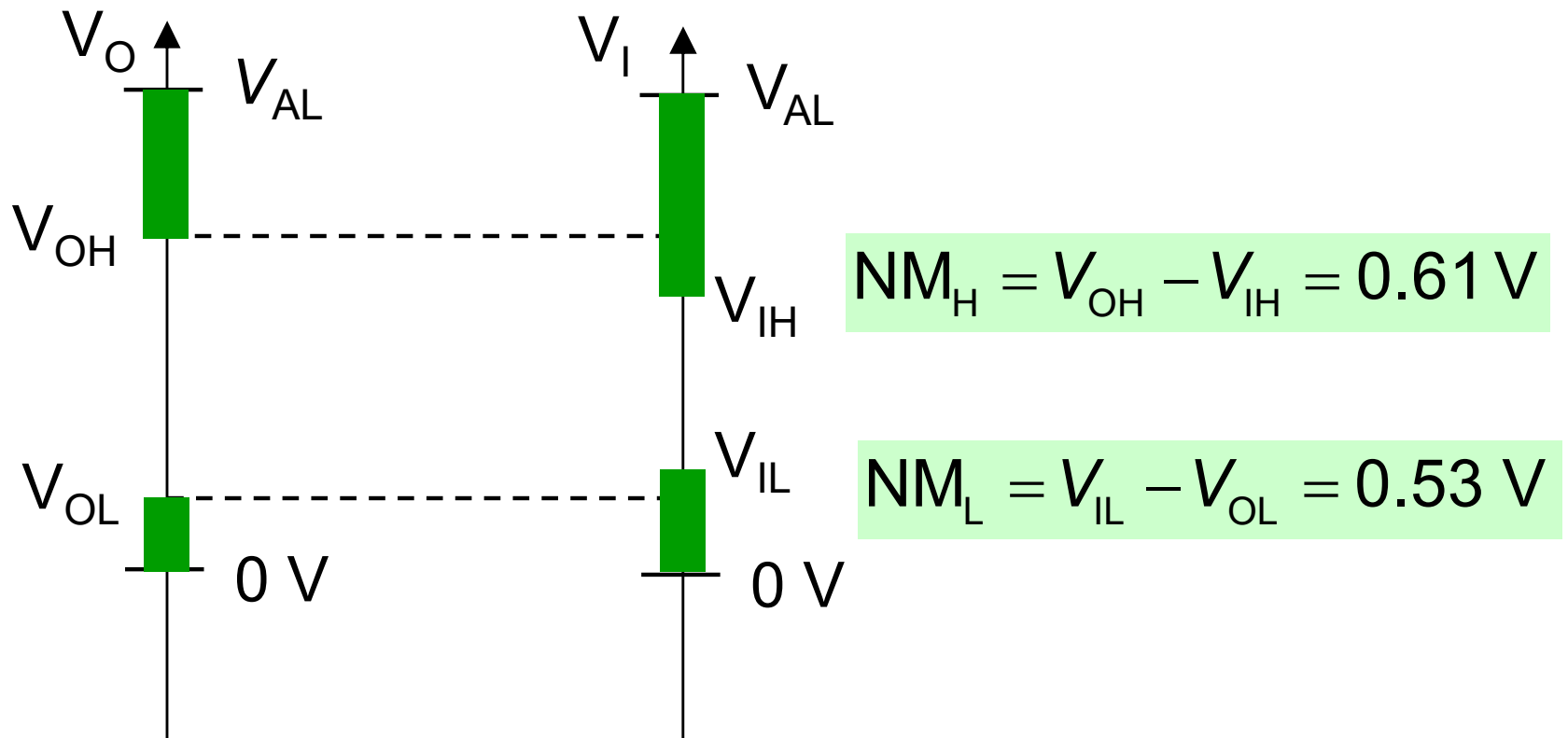
# Problem 1 Solution

Since  $NM_H$  and  $NM_L$  are positive we conclude that the ports **are compatible**



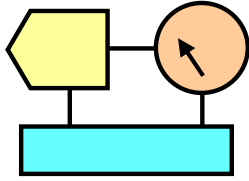

## Problem 2- Assignment

### Dynamic parameters

- a) Calculate the maximum delay ( $t_{DLH,max}$ ) in the connection of two gates with the following electrical parameters


$$V_{OL} = 0.4 \text{ V};$$
$$C_l = 50 \text{ pF}$$

$$V_{OH} = 3 \text{ V};$$
$$R_{OH,OL} = 130 \text{ } \Omega$$

$$V_{IL} = 1 \text{ V};$$
$$R_l = 1 \text{ M}\Omega$$

$$V_{IH} = 2 \text{ V};$$

 - b) Calculate how many gates can be connected to the output to limit the delay to 20 ns





## Problem 2


### Theoretical remind
  
#### Delay RC model: L→H transition of the output

The time needed for the output voltage  $V$  to reach the threshold voltage  $V_T$  starting from L level is the delay time  $t_{DLH}$



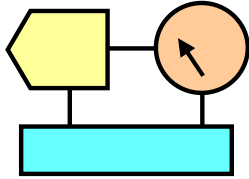$V_T$  is generally not known precisely. We only know that it is between  $V_{IL}$  and  $V_{IH}$ . Therefore, we can calculate a minimum delay for  $V_T = V_{IL}$  and a maximum delay for  $V_T = V_{IH}$



## Problem 2a Solution

The voltage  $V(t)$  is (charge of a capacitor with capacitance  $C_l$ ):

$$V(t) = V_{OH} + (V_{OL} - V_{OH})e^{-t/\tau_{LH}}$$

$$\left\{ \begin{array}{l} V(t=0) = 0 \\ V(t \rightarrow +\infty) = V_{DD} \end{array} \right.$$

with  $\tau_{LH} = C_l R_{OH} = 6.5 \text{ ns}$  ( $R_l$  can be neglected since it is  $\gg R_{OH}$ ).

Since the **maximum delay**  $t_{DLH,max}$  satisfies the relation  $V(t_{DLH,max}) = V_{IH}$ :

$$V_{IH} = V_{OH} (1 - e^{-t_{DLH,max}/\tau_{LH}})$$


$$t_{DLH,max} = \tau_{LH} \ln \left[ \frac{V_{DD}}{(V_{DD} - V_{IH})} \right]$$

**At the exam you  
could use this  
simplified formula**

NOTE: In the ideal case:  $V_{IH} = V_{IL} = V_T = \frac{V_{AL}}{2} \Rightarrow$
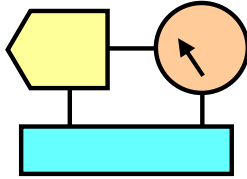
$$t_{DLH} = \ln(2) \tau_{LH} = 0.69 \times 6.5 \text{ ns} = 4.485 \text{ ns}$$





## Problem 2b Solution

The total delay increases in presence of  $n_{\text{gates}}$  ( $>1$ ) **gates** connected to the output because the total capacitance increases according to the formula:

$$C_{\text{tot}} = n_{\text{gates}} C_l$$

In fact:


$$\tau_{\text{LH}} = R_{\text{OH}} C_{\text{tot}} = n_{\text{gates}} (R_{\text{OH}} C_l) = n_{\text{gates}} 6.5 \text{ ns}$$


In the ideal case:

$$t_{\text{DLH}, n_{\text{gates}}} = \ln(2) \tau_{\text{LH}} = 0.69 n_{\text{gates}} 6.5 \text{ ns}$$

From which, in order to limit the delay to 20 ns ( $t_{\text{DLH}, n_{\text{gates}}} < 20 \text{ ns}$ ), we must require that:

$$n_{\text{gates}} < 4$$

 

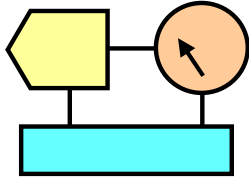


## Problem 3- Assignment

### Combinational logic circuit

- a) Plot the circuit in CMOS technology that implements the logic function:

$$U = (A*B) + C$$

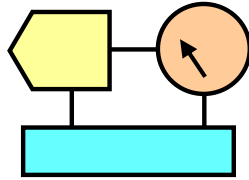- b) If the output is loaded with  $C_L = 50 \text{ pF}$ , calculate the maximum delay for a L- $\rightarrow$  H and H- $\rightarrow$  L transition. Assume for each MOS  $R_O = 60 \Omega$ .



# Problem 3

## Theoretical remind

---

### Boolean identities

#### AND function

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

$$A \cdot 0 = 0$$

$$0 \cdot A = 0$$

$$A \cdot 1 = A$$

$$1 \cdot A = A$$

$$A \cdot A = A$$

$$A \cdot a = 0$$

#### OR function

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

$$A + 0 = A$$

$$0 + A = A$$

$$A + 1 = 1$$

$$1 + A = 1$$

$$A + A = A$$

$$A + a = 1$$

#### NOT function

$$0 = 1$$

$$1 = 0$$

$$A = A$$

---

### Boolean laws

#### Commutative law

$$AB = BA$$

$$A + B = B + A$$

#### Absorption law

$$A + AB = A$$

$$A(A + B) = A$$

#### Distributive law

$$A(B + C) = AB + AC$$

$$A + BC = (A + B)(A + C)$$

#### De Morgan's law

$$a \overline{b} \overline{c} = a \cdot \overline{b} \cdot \overline{c}$$

$$a \overline{b} \overline{c} = a + \overline{b} + \overline{c}$$

#### Associative law


$$A(BC) = (AB)C$$

$$A + (B + C) = (A + B) + C$$

#### Note also

$$A + a \cdot B = A + B$$

$$A(a + B) = AB$$

 


## Problem 3a Solution


1. We define the **equivalent nSW structure** starting from the **negated output**.


From the De Morgan's laws and the other properties of the Boolean algebra:

$$U^* = ((A * B) + C)^*$$

 
 
$$U^* = (A * B)^* C^* = (A + B^*) C^* = A C^* + B^* C^*$$



 

## Problem 3a Solution

1. We define the **equivalent nSW structure** starting from the **negated output**.



From the De Morgan's laws and the other properties of the Boolean algebra:


$$U^* = ((A^*B) + C)^*$$



$$U^* = (A^*B)^* C^* = (A + B^*) C^* = A C^* + B^* C^*$$

  
2. We define the **complementary pSW circuit**




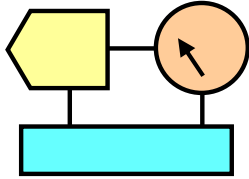

## Problem 3a Solution


3. We build the **complete circuit**

 


 
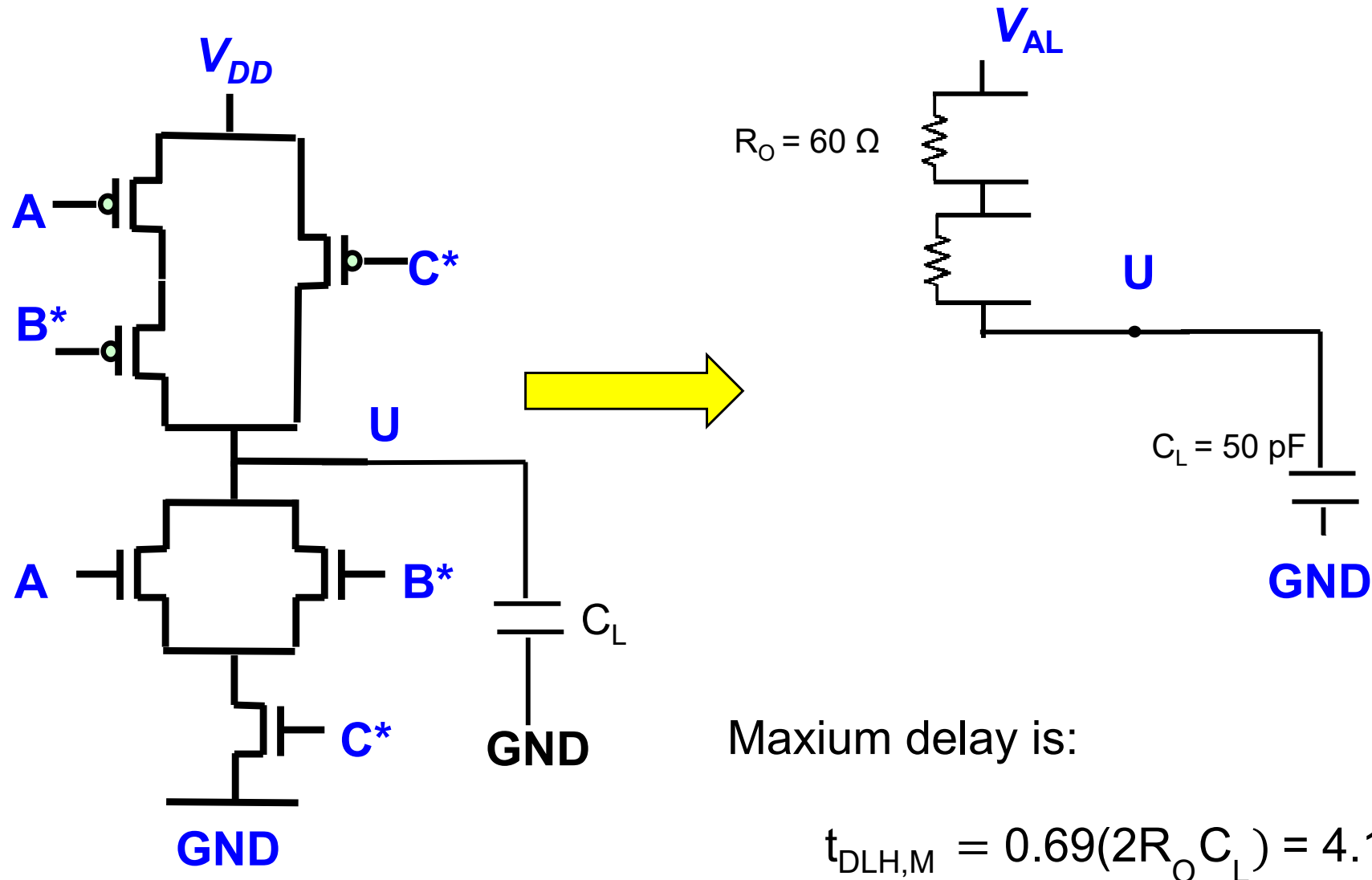
## Problem 3b Solution

**Delay for L→H:** we use the simplified formula for the delay time:  $t_{DLH} = 0.69\tau_{LH}$






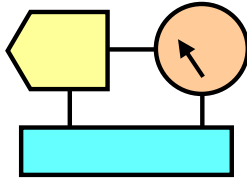

## Problem 3b Solution

**Delay for  $H \rightarrow L$ :** we use the simplified formula for the delay time:


$$t_{DHL} = 0.69\tau_{HL}$$

  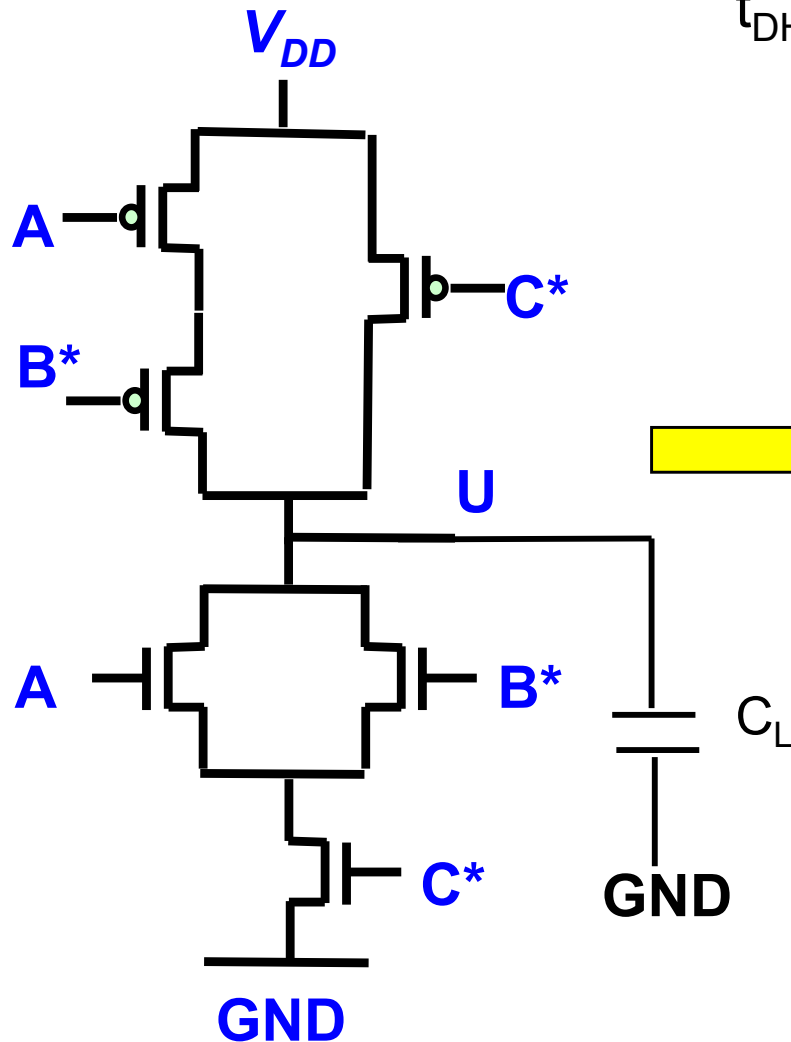

maximum delay is:
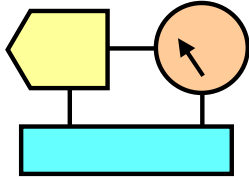
$$t_{DHL,M} = 0.69(2R_O C_L) = 4.1 \text{ ns}$$





## Problem 4 - Assignment


### Power consumption

a) Calculate the static and dynamic power consumption of a CMOS circuit with:

- Voltage supply of 2 V
- In average per time instant:
  - 50.000.000 transistors in 'off' state
  - 100.000.000 inputs with  $C_i = 1$  fF

Consider the two cases:

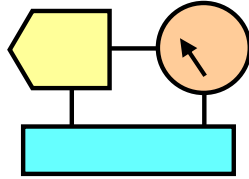- Switching frequency  $F_m = 200$  MHz and  $I_{off} = 1$  nA per MOS
- Switching frequency  $F_m = 2$  GHz and  $I_{off} = 100$  nA per MOS



## Problem 4a Solution

The **static power dissipated** due to  $I_{off}$  of the MOS transistors is:

$P_S = I_{off} \times 2V \times N_{off}$  where  $N_{off}$  is the number of transistors OFF.

Then: for  $I_{off} = 1 \text{ nA}$  and  $N_{off} = 50E6$ :

for  $I_{off} = 100 \text{ nA}$  and  $N_{off} = 50E6$ :

$$\begin{aligned} P_S &= 0.1 \text{ W} \\ P_S &= 10 \text{ W} \end{aligned}$$

The **dynamic power dissipated** due to capacitance charge/discharge is:

$P_D = (C \times F_m \times V^2) \times N$  where  $N$  is the number of connected transistors.


Then for a single transistor connected we get:

for  $F_m = 200 \text{ MHz}$ :  $P_D (1 \text{ capacitor, } 200 \text{ MHz}) = 0.8 \text{ } \mu\text{W}$

for  $F_m = 2 \text{ GHz}$ :  $P_D (1 \text{ capacitor, } 2 \text{ GHz}) = 8.0 \text{ } \mu\text{W}$

Finally, multiplying by the number of transistors  $N = 100E6$  we get:
 
$$P_D (\text{total, } 200\text{MHz}) = 80 \text{ W and } P_D (\text{total, } 2 \text{ GHz}) = 800 \text{ W}$$





## Problem 5 - Assignment


### Sequential logic circuits

### Timing diagrams

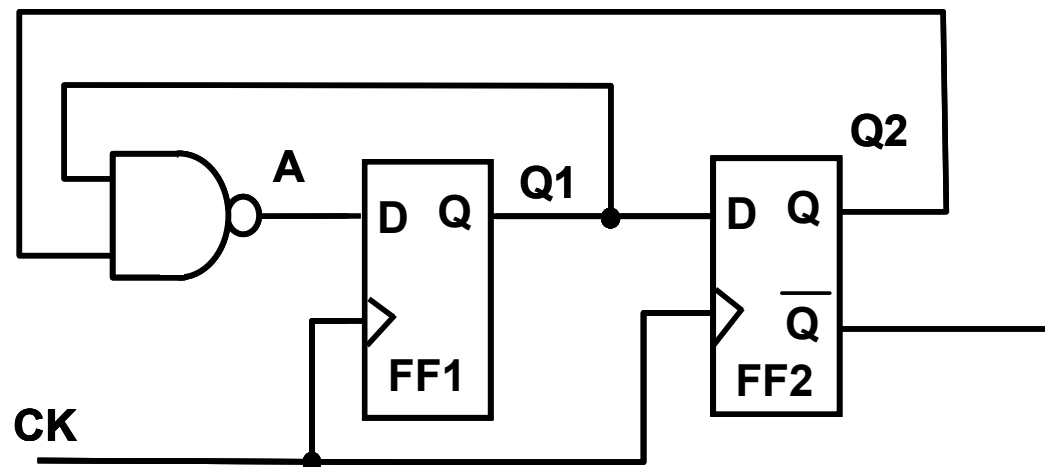- a) Plot in a timing diagram the output signals sequence ( $Q_1(t)$ ;  $Q_2(t)$ ;  $A(t)$ ) for 4 clock cycles in the digital circuit reported in the picture below. Assume that at the initial state ( $t = 0$ ):  $Q_i = 0$
- b) Compute the delays and estimate the maximum clock frequency in the case:  $T_{\text{NAND}} = 2 \text{ ns}$  ;  $T_{\text{CKQ}} = 3 \text{ ns}$ ;  $T_{\text{su}} = 1 \text{ ns}$  ;  $T_{\text{h}} = 1 \text{ ns}$



 


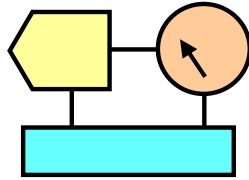

## Problem 5b Solution

$$T_{\text{NAND}} = 2 \text{ ns} ; T_{\text{CKQ}} = 3 \text{ ns} ; T_{\text{su}} = 1 \text{ ns} ; T_{\text{h}} = 1 \text{ ns}$$

- Signals sequences (with delays)

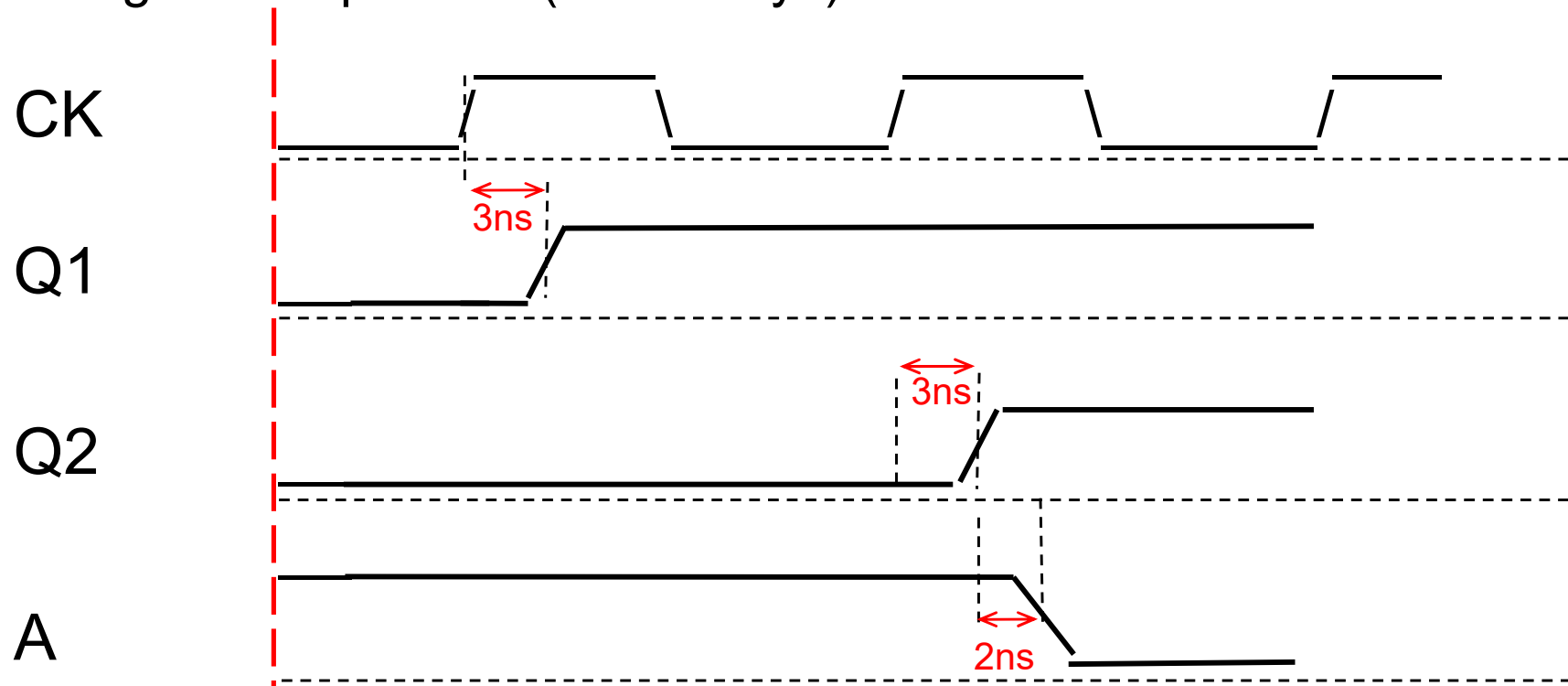

Guide for the eye


The most stringent time constraint on the clock period  $T_{\text{CK}}$  is:


$$T_{\text{CK}} > T_{\text{CK} \rightarrow \text{Q}} + T_{\text{su}} + T_{\text{NAND}} = 6 \text{ ns}$$

The **maximum clock frequency**  $F_{\text{CKmax}}$   
is thus:

$$F_{\text{CKmax}} = 167 \text{ MHz}$$

Digital circuit

 

 


## Problem 6 - Assignment

### Sequential logic circuits
 
### Timing diagrams

Consider the circuit shown in the figure. The FF outputs are initially set at 0; I1 and I2 have an open drain output.



- a) Plot for at least two clock cycles the time diagrams at the nodes  $Q_1, Q_2, Q_3$  and  $V_c$  quoting the delays and consider the following parameters:


CK period  $T_{CK} = 24 \text{ ns}$ ,  $C = 0$

FF D:  $T_{CKQ} = 4 \text{ ns}$  (both transitions),  $T_{su} = 2 \text{ ns}$ ,  $T_h = 3 \text{ ns}$

FF JK:  $T_{CKQ} = 3 \text{ ns}$  (both transitions),  $T_{su} = 3 \text{ ns}$ ,  $T_h = 2 \text{ ns}$


I1 and I2 inverter:  $T_{LH1} = 6 \text{ ns}$ ,  $T_{HL1} = 1 \text{ ns}$

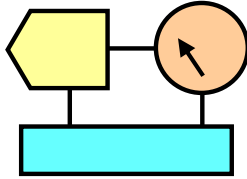I3 inverter:  $T_{LH3} = 3 \text{ ns}$ ,  $T_{HL3} = 4 \text{ ns}$




**Cont.**

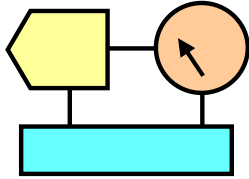- c) Given the parameters of b), calculate the maximum clock frequency (consider  $C = 0$ ).
- d) Substitute I3 with a non-inverting buffer and move the input of I3 from  $Q_2$  to  $V_c$ . Calculate in this new configuration the maximum clock frequency (with  $C = 0$  and same parameters as in b). Discuss how  $C \neq 0$  changes the maximum clock frequency.



 
## Problem 6a,b Solution

- The system has a feedback **loop with two FFs**, therefore the system evolves in a cycle with 4 states maximum.









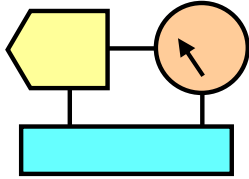
 
## Problem 6a,b Solution


- The system has a feedback **loop with two FFs**, therefore the system evolves in a cycle with 4 states maximum.
- The clock is active in the **L-H transition in the FF1** and in the **H-L transition in the FF2**, therefore a cycle with the evolution through all the 4 states is concluded in two CK periods.
- The node  $V_c$  is a **wired-AND** of  $Q_1$  and  $Q_2^*$ , therefore  $V_c$  is High only when we have the state  $Q_1 = 1$  and  $Q_2 = 0$ . In the other 3 states of  $Q_1, Q_2$ , we have one of the outputs of I1 or I2 in the high impedance (HZ) state (I1 when  $Q_1 = 0$ , I2 when  $Q_2 = 1$ ). In these cases the voltage  $V_c$  is determined by the connection to GND of the other output (I2 when I1 is HZ, I1 when I2 is HZ).




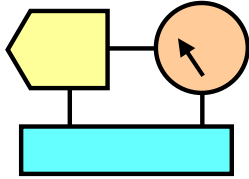
 
## Problem 6a,b Solution


- The system has a feedback **loop with two FFs**, therefore the system evolves in a cycle with 4 states maximum.
- The clock is active in the **L-H transition in the FF1** and in the **H-L transition in the FF2**, therefore a cycle with the evolution through all the 4 states is concluded in two CK periods.
- The node  $V_c$  is a **wired-AND** of  $Q_1$  and  $Q_2^*$ , therefore  $V_c$  is High only when we have the state  $Q_1 = 1$  and  $Q_2 = 0$  ( $Q_2^* = 1$ ). In the other 3 states of  $Q_1, Q_2$ , we have one of the outputs of I1 or I2 in the high impedance (HZ) state (I1 when  $Q_1 = 0$ , I2 when  $Q_2 = 1$ ). In these cases the voltage  $V_c$  is determined by the connection to GND of the other output (I2 when I1 is HZ, I1 when I2 is HZ).
- **FF3 is not part of the feedback loop**, therefore the output is only dependent on the voltage on  $V_c$ . Q3 changes the state (on the CK transition H->L) only when  $V_c$  is High.



 

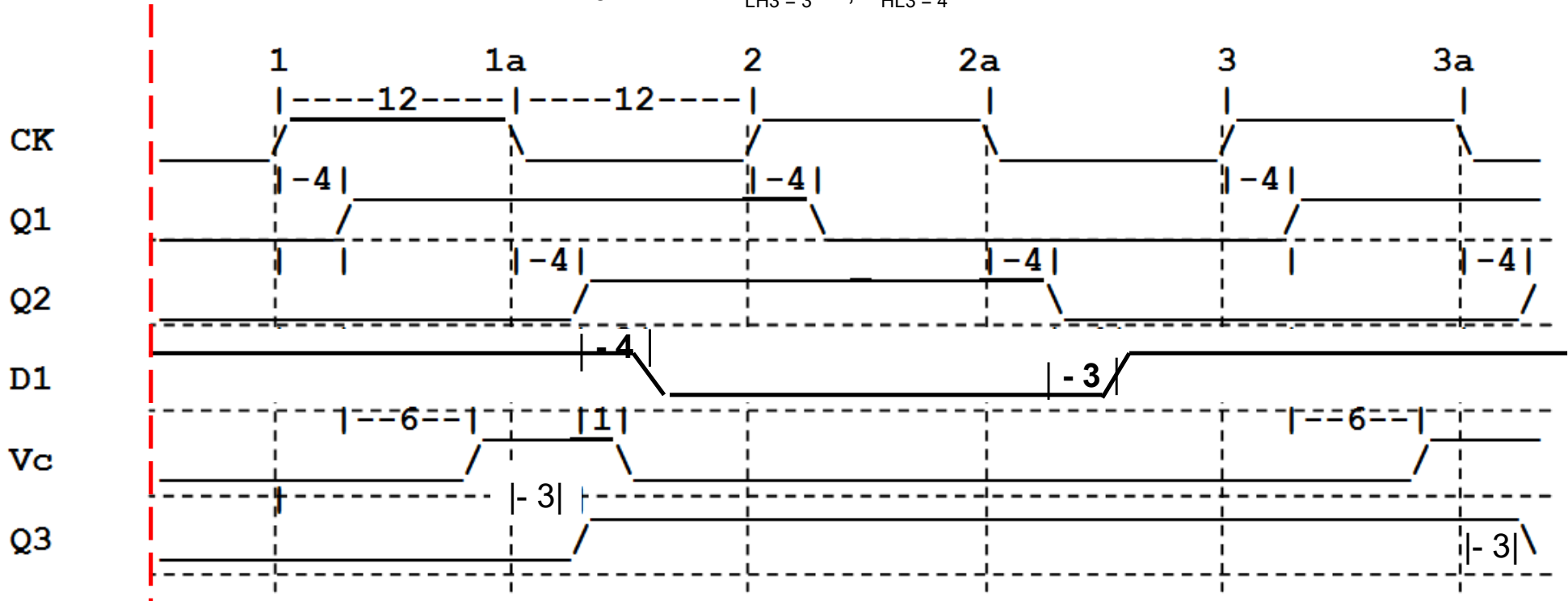
## Problem 6a,b Solution


CK period  $T_{CK} = 24 \text{ ns}$ ,  $C=0$   
FF D:  $T_{CKQ} = 4 \text{ ns}$  (both transitions)  
FF JK:  $T_{CKQ} = 3 \text{ ns}$  (both transitions)  
I1 and I2 inverter:  $T_{LH1} = 6 \text{ ns}$ ,  $T_{HL1} = 1 \text{ ns}$   
I3 inverter:  $T_{LH3} = 3 \text{ ns}$ ,  $T_{HL3} = 4 \text{ ns}$



Guide for the eye

Digital circuit

 


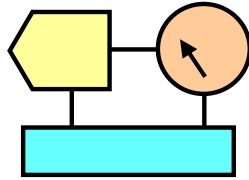



## Problem 6c Solution

Considering the 3 FFs, we set constrain on  $T_{CK}$  or on  $T_{CK}/2$  such that the set-up conditions are satisfied at each FF. For this circuit we have therefore **3 constrains** and the **maximum CK frequency is determined by the most stringent one** (i.e: the worst case). The worst case corresponds to the path producing the maximum delay across the combinational logic network.
  
### Set-up constrain at FF1:

The data D is obtained by the output  $Q_2$  (present after the H->L CK transition) and further delayed by I3 as shown in the following scheme:



 

## Problem 6c Solution

As consequence we have that the maximum delay across the FF2 + combinational logic network must be lower than  $T_{CK}/2$  minus the set-up time:

$$T_{CKQFF2} + T_{dmaxl3} < \frac{T_{CK}}{2} - T_{suFF1} \quad (\text{eq. 1})$$


Then, we get:

$$T_{CK} > 2 (T_{CKQFF2} + T_{HL3} + T_{suFF1})$$

Note that:

- We use for  $T_{dmaxl3}$  the propagation time  $T_{HL3}$  because it the longest one
- We have the factor 2 because the FF1 and FF2 are active on different CK edges; if they where active on the same edge, eq. (1) would have applied over a CK period and not over a half-period.

 With the given values:  $T_{CK} > 2 (4 \text{ ns} + 4 \text{ ns} + 2 \text{ ns}) = 20 \text{ ns}$



## Problem 6c Solution

### Set-up constrain at FF2:

In a similar way we write in eq. (2) the set-up condition for FF2. This is less stringent than eq. (1), because we do not have any additional delay over any combinational network (i.e: the input D of FF2 is directly  $Q_1$  of FF1).  $Q_1$  switches at the CK transition L→H after a delay  $T_{CKQFF1}$ , therefore:

$$T_{CKQFF1} < \frac{T_{CK}}{2} - T_{suFF2} \Rightarrow T_{CK} > 2(4 \text{ ns} + 2 \text{ ns}) = 12 \text{ ns} \quad (\text{eq. 2})$$

### Set-up constrain at FF3:


In this case the delays to consider are the one through FF1 and the inverter I1 or through FF2 and the inverter I2.

We get as the most stringent constraint:

$$T_{CKQFF1} + T_{dmaxI1} < \frac{T_{CK}}{2} - T_{suFF3} \Rightarrow T_{CK} > 2(4 \text{ ns} + 6 \text{ ns} + 3 \text{ ns}) = 26 \text{ ns} \quad (\text{eq. 3})$$

In conclusion the most stringent constrain on  $T_{CK}$  is given by eq. (3) with

 $T_{CK} > 26 \text{ ns}$  and then the **maximum CK frequency** is:  $F_{CKmax} = 38.5 \text{ MHz}$



## Problem 6d Solution


Moving the input of I3 to the node Vc, we add an additional delay due to I2. The set-up condition for FF1 becomes:

$$T_{CKQFF2} + T_{dmaxI3} + T_{dmaxI2} < \frac{T_{CK}}{2} - T_{suFF1} \quad (\text{eq. 1})$$

Therefore we obtain:  $T_{CK} > 2 (4 \text{ ns} + 4 \text{ ns} + 6 \text{ ns} + 2 \text{ ns}) = 32 \text{ ns}$  and then the maximum frequency becomes:  $F_{CKmax} = 31.25 \text{ MHz}$

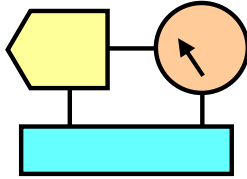The capacitor C (neglected in the previous points of this exercise) causes an increased delay due to the increase of both  $T_{HL1}$  and  $T_{LH1}$  and reduces the  $F_{CKmax}$ .






## Problem 7 – Assignment

### Finite State Machine

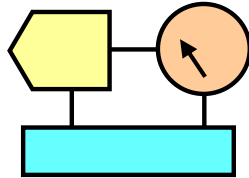
- a) Design a FSM (Finite State Machine) that acts as 2 bit counter triggered by an input signal T (i.e: the counter advances of 1 (base 10) every time  $T = 1$ ; the counter does not advance if  $T=0$ )
- b) Calculate the maximum CK frequency




## Problem 7a Solution

2 bit counter  $\Rightarrow$  number of different states:  $2^2 = 4$


FSM states:

 


STATE	$Q_1$	$Q_0$	
A	0	0	Out = 0
B	0	1	Out = 1
C	1	0	Out = 2
D	1	1	Out = 3

 

# Problem 7a Solution FSM machine bocks

 

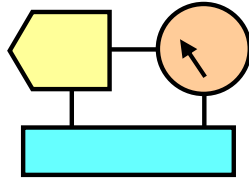


## Problem 7a Solution


### Next state (Future state) circuit

The circuit generates the future state (represented by  $D_0, D_1$ ) given the current state (represented by  $Q_0$  and  $Q_1$ )

- If  $T=0 \rightarrow$  the circuit remains in the current state
- If  $T=1 \rightarrow$  current state +1 (the circuit moves to next state)
- Circuit: Adder controlled by  $T$
 
$$\begin{aligned} D_0 &= Q_0 \text{ XOR } T \\ C_1 &= Q_0 \text{ AND } T \\ D_1 &= Q_1 \text{ XOR } C_1 \end{aligned}$$



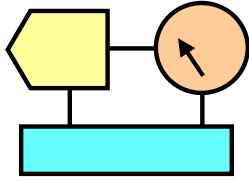


# Problem 7a Solution Adder circuit


$$\text{OUT} = Q_1 2^1 + Q_0 2^0 = 0 \cdot 2^1 + 1 \cdot 2^0 = 1 = B$$

$$\text{OUT} = D_1 2^1 + D_0 2^0 = 0 \cdot 2^1 + 1 \cdot 2^0 = 1 = B$$

XOR truth table

Input		Output
A	B	
0	0	0
0	1	1
1	0	1
1	1	0

 

 


# Problem 7a Solution Adder circuit


$$\text{OUT} = Q_1 2^1 + Q_0 2^0 = 0 \cdot 2^1 + 1 \cdot 2^0 = 1 = B$$

$$\text{OUT} = D_1 2^1 + D_0 2^0 = 1 \cdot 2^1 + 0 \cdot 2^0 = 2 = C$$


XOR truth table


Input		Output
A	B	
0	0	0
0	1	1
1	0	1
1	1	0

 

 


# Problem 7a Solution FSM machine bocks

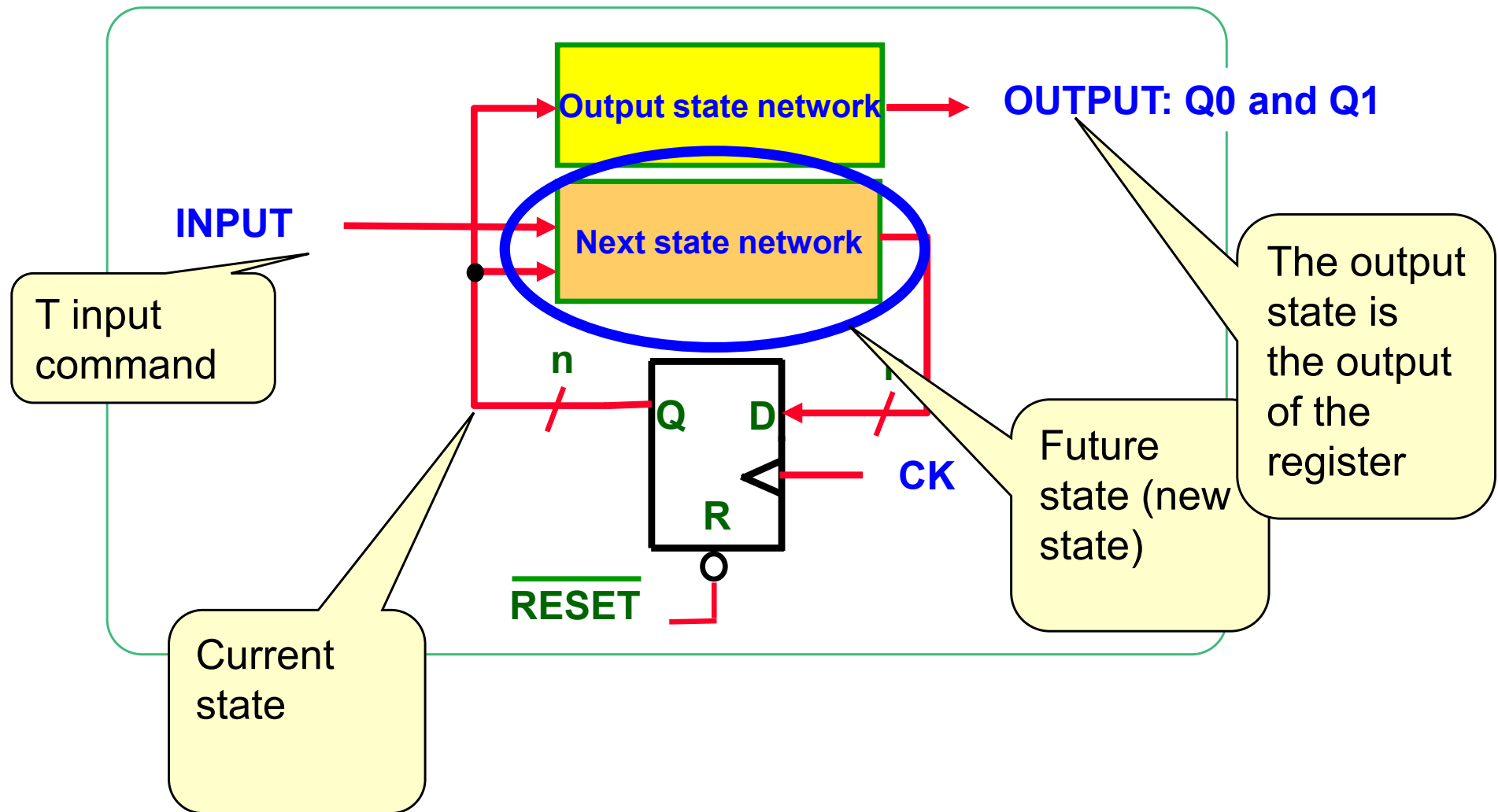


 
 
# Problem 7a Solution FSM machine: final circuit





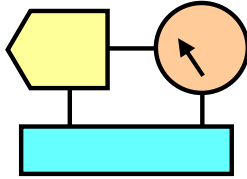

## Problem 7b Solution Maximum operation frequency


The maximum operation frequency  $F_{CKmax} = 1/T_{CKmin}$  is linked to:

- FF Delay CK  $\rightarrow$  Q:  $T_{CKQ}$
- Combinational circuit delay:  $T_{CL}$
- FF set up time:  $T_{su}$

Than:

$$T_{CKQ} + T_{CLmax} + T_{su} = T_{CKmin}$$


Since the next state logic is:

 


$$\begin{aligned} D_0 &= Q_0 \text{ XOR } T \\ C_1 &= Q_0 \text{ AND } T \\ D_1 &= Q_1 \text{ XOR } C_1 \end{aligned}$$

we get:

$$T_{CLmax} = T_{AND} + T_{XOR}$$

 

 

# Problem - Assignment

## Square wave generator


Design a square wave generator with frequency 50 KHz using a Schmitt trigger inverter 74HC14

### SN54HC14, SN74HC14 HEX SCHMITT-TRIGGER INVERTERS


SCLS085E – DECEMBER 1982 – REVISED NOVEMBER 2004

- Wide Operating Voltage Range of 2 V to 6 V
- Outputs Can Drive Up To 10 LSTTL Loads
- Low Power Consumption, 20- $\mu$ A Max  $I_{CC}$
- Typical  $t_{pd} = 11$  ns
- $\pm 4$ -mA Output Drive at 5 V
- Low Input Current of 1  $\mu$ A Max

 SN54HC14 . . . J OR W PACKAGE  
SN74HC14 . . . D, DB, N, NS, OR PW PACKAGE  
(TOP VIEW)




SN54HC14 . . . FK PACKAGE  
(TOP VIEW)

 


NC – No internal connection
 
#### description/ordering information

These Schmitt-trigger devices contain six independent inverters. They perform the Boolean function  $Y = \bar{A}$  in positive logic.



 
# Transcharacteristic of the Schmitt trigger




## • 74HC14

- Thresholds  $V_{T\pm}$  is dependent on supply voltage  $V_{CC}$
- Values spread in a wide range

SYMBOL	PARAMETER	T <sub>amb</sub> (°C)							UNIT	TEST
		74HCT								V <sub>CC</sub> (V)
		+25			−40 to +85		−40 to +125			
		min.	typ.	max.	min.	max.	min.	max.		
V <sub>T+</sub>	positive-going threshold	1.2 1.4	1.41 1.59	1.9 2.1	1.2 1.4	1.9 2.1	1.2 1.4	1.9 2.1	V	4.5 5.5
V <sub>T−</sub>	negative-going threshold	0.5 0.6	0.85 0.99	1.2 1.4	0.5 0.6	1.2 1.4	0.5 0.6	1.2 1.4	V	4.5 5.5
V <sub>H</sub>	hysteresis (V <sub>T+</sub> −V <sub>T−</sub> )	0.4 0.4	0.56 0.60	— —	0.4 0.4	— —	0.4 0.4	— —	V	4.5 5.5

 


 

# Problem
 
## Theoretical remind

Binary signal: periodic repetition  
of high and low levels



Parameters:

Voltage levels:

$V_H, V_L$

Period:


$T$

Frequency:

$f = 1/T$

Duty Cycle:


$DC = T_H/T$

 

## Digital Circuit for the generation of square wave signal:

- ANALYSIS
- DESIGN

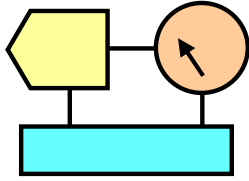Example: it can be used to generate the **clock signal (CK)** for digital counters



- The low pass RC filter is driven by a digital signal (input to  $V_H$  or  $V_L$ )

The capacitor is charged/discharged with exponential law


1. Capacitor discharge ( $t=0$ ,  $V_C = V_H$ )


$$V(t) = V_H e^{-t/RC} \quad (V_L = 0)$$

2. Capacitor charge ( $t=0$ ,  $V_C = V_L = 0$ )

$$V(t) = V_H (1 - e^{-t/RC})$$


## 1 ingredient: RC filter

 

 


 
## 2 ingredient: Comparator circuit

- The voltage  $V_C$  is compared with the **comparator** thresholds
  - The **comparator**, i.e. **Schmitt trigger inverter**, has hysteresis




 - The output of the comparator drives the RC circuit




 

## Square wave oscillator

 


 The capacitor is **charged** or **discharged** by the output current of the trigger comparator. The capacitor voltage varies between  $V_{s1}$  and  $V_{s2}$




 Assume that at  $t=0$ :  $V_C = 0 \Rightarrow$  no charge on the capacitance  $\Rightarrow V_U = V_{UH}$







## Square wave oscillator

 

 The capacitor is **charged** or **discharged** by the output current of the trigger comparator. The capacitor voltage varies between  $V_{s1}$  and  $V_{s2}$




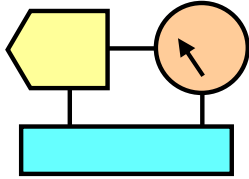Assume that at  $t=0$ :  $V_C = 0 \Rightarrow$  no charge on the capacitance  $\Rightarrow V_U = V_{UH}$




# Problem Solution

## Calculation of the square wave period

 


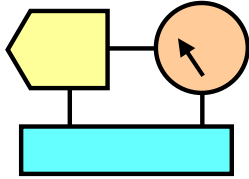Since the voltage across the capacitor is:  $V_C(t) = V_{UL} - (V_{UL} - V_{S2})e^{-t/RC}$



# Problem Solution


## Calculation of the square wave period

 

$$V_C(t) = V_{oL} - (V_{oL} - V_{S2})e^{-t/RC}$$


Then the  $T'$  interval is given by:
 
$$V_{S1} = V_{oL} - (V_{oL} - V_{S2})e^{-T'/RC} \Rightarrow T' = RC \ln \left[ \frac{(V_{oL} - V_{S2})}{(V_{oL} - V_{S1})} \right]$$




# Problem Solution

## Calculation of the square wave period

 


Since the voltage across the capacitor is:
 
$$V_C(t) = V_{oH} - (V_{oH} - V_{S1})e^{-t/RC}$$



# Problem Solution


## Calculation of the square wave period

 

$$V_C(t) = V_{oH} - (V_{oH} - V_{S1})e^{-t/RC}$$

Then the  $T''$  interval is given by:
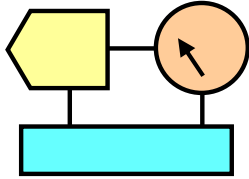
$$V_{S2} = V_{oH} - (V_{oH} - V_{S1})e^{-T''/RC} \Rightarrow T'' = RC \ln \left[ \frac{(V_{oH} - V_{S1})}{(V_{oH} - V_{S2})} \right]$$





# Problem Solution


## Calculation of the square wave period

Finally we get:

$$T = T' + T'' = RC \ln \left[ \frac{(V_{oL} - V_{S2})}{(V_{oL} - V_{S1})} \right] + RC \ln \left[ \frac{(V_{oH} - V_{S1})}{(V_{oH} - V_{S2})} \right]$$

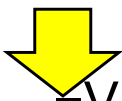 
$$T = RC \ln \left[ \frac{(V_{oL} - V_{S2})(V_{oH} - V_{S1})}{(V_{oL} - V_{S1})(V_{oH} - V_{S2})} \right]$$



 

# Problem Solution

## Calculation of the square wave period

### SN54HC14, SN74HC14 HEX SCHMITT-TRIGGER INVERTERS

SCLS085E - DECEMBER 1982 - REVISED NOVEMBER 2004

electrical characteristics over recommended operating free-air temperature range (unless otherwise noted)

PARAMETER	TEST CONDITIONS		V <sub>CC</sub>	T <sub>A</sub> = 25°C			SN54HC14		SN74HC14		UNIT	
				MIN	TYP	MAX	MIN	MAX	MIN	MAX		
V <sub>T+</sub>			2 V	0.7	1.2	1.5	0.7	1.5	0.7	1.5	V	
			4.5 V	1.55	2.5	3.15	1.55	3.15	1.55	3.15		
			6 V	2.1	3.3	4.2	2.1	4.2	2.1	4.2		
V <sub>T-</sub>			2 V	0.3	0.6	1	0.3	1	0.3	1	V	
			4.5 V	0.9	1.6	2.45	0.9	2.45	0.9	2.45		
			6 V	1.2	2	3.2	1.2	3.2	1.2	3.2		
V <sub>T+</sub> - V <sub>T-</sub>			2 V	0.2	0.6	1.2	0.2	1.2	0.2	1.2	V	
			4.5 V	0.4	0.9	2.1	0.4	2.1	0.4	2.1		
			6 V	0.5	1.3	2.5	0.5	2.5	0.5	2.5		
V <sub>OH</sub>	V <sub>I</sub> = V <sub>IH</sub> or V <sub>IL</sub>	I <sub>OH</sub> = -20 μA	2 V	1.9	1.998		1.9		1.9	V		
			4.5 V	4.4	4.499		4.4		4.4			
			6 V	5.9	5.999		5.9		5.9			
			I <sub>OH</sub> = -4 mA	4.5 V	3.98	4.3		3.7			3.84	
			I <sub>OH</sub> = -5.2 mA	6 V	5.48	5.8		5.2			5.34	
V <sub>OL</sub>	V <sub>I</sub> = V <sub>IH</sub> or V <sub>IL</sub>	I <sub>OL</sub> = 20 μA	2 V		0.002	0.1		0.1		0.1	V	
			4.5 V		0.001	0.1		0.1		0.1		
			6 V		0.001	0.1		0.1		0.1		
			I <sub>OL</sub> = 4 mA	4.5 V		0.17	0.26		0.4			0.33
			I <sub>OL</sub> = 5.2 mA	6 V		0.15	0.26		0.4			0.33
I <sub>I</sub>	V <sub>I</sub> = V <sub>CC</sub> or 0	6 V		±0.1	±100		±1000		±1000	nA		
I <sub>CC</sub>	V <sub>I</sub> = V <sub>CC</sub> or 0, I <sub>O</sub> = 0	6 V			2		40		20	μA		
C <sub>i</sub>			2 V to 6 V		3	10		10		10	pF	

switching characteristics over recommended operating free-air temperature range, C<sub>L</sub> = 50 pF (unless otherwise noted) (see Figure 1)

PARAMETER	FROM (INPUT)	TO (OUTPUT)	V <sub>CC</sub>	T <sub>A</sub> = 25°C			SN54HC14		SN74HC14		UNIT
				MIN	TYP	MAX	MIN	MAX	MIN	MAX	
t <sub>pd</sub>	A	Y	2 V		55	125		190		155	ns
			4.5 V		12	25		38		31	
			6 V		11	21		32		26	
t <sub>t</sub>		Y	2 V		38	75		110		95	ns
			4.5 V		8	15		22		19	
			6 V		6	13		19		16	

operating characteristics, T<sub>A</sub> = 25°C

PARAMETER	TEST CONDITIONS	TYP	UNIT
C <sub>pd</sub> Power dissipation capacitance per inverter	No load	20	pF

From the Datasheet for V<sub>CC</sub> = 4.5 V:

$$V_{T-} = V_{S1} = 1.6V$$

$$V_{T+} = V_{S2} = 2.5V$$

$$V_{OH} = 4.3V$$

$$V_{OL} = 0.17V$$



In order to have a square wave frequency of 50 kHz that corresponds to T = 1/50 ms = 20 μs we then must require that:

$$RC \cong 22 \mu s \xRightarrow{\text{e.g.}} \begin{cases} R = 10 \text{ k}\Omega \\ C = 2.22 \text{ nF} \end{cases}$$